

Lab 1 Results –Intro to DC Circuits

ECE202: Fundamentals of Electrical Engineering

Name	Student ID	CCID
Misbah Ahmed Nauman	1830574	misbahah
Muhammad Abdur Rab Siddiqui	1804733	msiddiq6

2.1 Equipment Familiarization

2.1.5.1

Measure Resistance						
	R1	R2	R3	R4	R5	R6
	10 Ω	100 Ω	470 Ω	1.0k Ω	4.7k Ω	10M Ω
Color 1	Brown	Brown	Yellow	Brown	Yellow	Brown
Color 2	Black	Black	Purple	Black	Purple	Black
Color 3	Black	Brown	Brown	Red	Red	Blue
Color 4	Golden	Golden	Golden	Golden	Golden	White
Color 5	Brown	NA	NA	NA	NA	NA
Tolerance(%)	1	5	5	5	5	5
R (Ω)	10.1	97.8	463	977	4564	10170

Measure Series Resistors		
RS1	RS2	RS3
100 Ω + 470 Ω	1.0k Ω + 4.7k Ω	10M Ω + 10M Ω
556.5 Ω	5.616 k Ω	20.62 M Ω

Measure Parallel Resistors		
RP1	RP2	RP3
100Ω // 470Ω	1.0kΩ // 4.7kΩ	10MΩ // 10MΩ
80.7	0.810 kΩ	5.15 MΩ

2.2 Ohm's Law and Power

470 Ω - Resistor							
Voltage	(V)	5.0	3.5	1.0	0	-2.5	-5.0
Voltage	(V)	4.9669	4.3821	1.0105	0.02	-2.456	-4.9325
Current	(mA)	10.7	7.48	2.13	0.00	-5.33	-10.69
Resistance	(Ω)	464.2	585.84	474.41	inf	460.8	461.4
Power	(mW)	0.0531	0.0328	0.00215	0.00	0.0131	0.0527
1.0 kΩ – Resistor							
Voltage	(V)	5.0	3.5	1.0	0	-2.5	-5.0
Voltage	(V)	4.9898	3.5001	1.015	0.023	-2.4686	-4.9577
Current	(mA)	5.05	3.54	1.010	0.00	-2.52	-5.06
Resistance	(Ω)	988.08	988.73	1004.95	Inf	979.6	979.78
Power	(mW)	0.0252	0.0124	0.00103	0.00	0.00622	0.0251
4.7 kΩ – Resistor							
Voltage	(V)	5.0	3.5	1.0	0	-2.5	-5.0
Voltage	(V)	5.0076	3.5143	1.0187	0.0234	-2.4732	-4.9766
Current	(mA)	1.08	0.76	0.21	0.00	-0.55	-1.09
Resistance	(Ω)	4636.0	4624.1	4851.0	inf	4496.7	4565.7
Power	(mW)	0.00541	0.00267	0.000214	0.00	0.00136	0.00542

2.3 Voltage Divider

R1	(Ω)	470			
R2	(Ω)	100	470	1.0 k	4.7 k
VS	(V)	5	5	5	5
IS	(mA)	8.80	5.38	3.44	0.99
V1	(V)	4.0925	2.51	1.6146	0.480
V2	(V)	0.855	2.4583	3.3657	4.5131
P_{R1}	(mW)	36.0	13.5	5.55	0.475
P_{R2}	(mW)	7.52	13.2	11.6	4.47
P_{Total}	(mW)	43.5	26.7	17.2	4.95

1. In the voltage divider circuit show your work for finding P_{R1} and P_{R2} for the case $R1 = 470 \Omega$ and $R2 = 1.0 \text{ k}\Omega$.

$$P_{R1} = V1 * IS = 1.6146 \text{ V} * 3.44 \text{ mA} = 5.55 \text{ mW}$$

$$P_{R2} = V2 * IS = 3.3657 \text{ V} * 3.44 \text{ mA} = 11.6 \text{ mW}$$

2.4 Current Divider

R1	(Ω)	470			
R2	(Ω)	100	470	1.0 k	4.7 k
VS	(V)	5.0048	5.0021	5.0064	5.0028
IS	(mA)	5.13	5.13	5.13	5.13
I1	(mA)	0.88	2.53	3.46	4.63
I2	(mA)	4.20	2.55	1.62	0.46
P_{R1}	(mW)	4.40	12.7	17.3	23.2
P_{R2}	(mW)	21.0	12.8	8.1	2.30
P_{Total}	(mW)	25.4	25.4	25.4	25.4

2.5 Potentiometer Divider

V1 Set-Point	(V)	0	1.0	2.5	4.0	5.0
V1	(V)	0.0146	1.0731	2.4678	3.9903	4.9920
V2	(V)	4.9623	3.9063	2.5133	0.9935	0.0067
IS	(mA)	4.66	4.66	4.66	4.66	4.66
V_{Total}	(V)	4.9769	4.9794	4.9811	4.9838	4.9987

2.6 Voltmeter Loading

V2	(V)	1.659
-----------	-----	-------

V1	(V)	1.678
VS	(V)	5.011
V2 + V1	(V)	3.337

2.6 Ammeter Loading

VS	(V)	0.5	1.5	2.5
IS	(mA)	34.72	103.7	172.7
V_(AMMETER)	(V)	0.132	0.367	0.607
R_{DMM}	(Ω)	3.80	3.54	3.51

2. Resistors typically have two important ratings: its resistance and its wattage. Explain how this wattage rating affects the amount of the voltage that can be applied to the resistor. Consider a 100Ω resistor with 0.25watt power rating.

Wattage can be used to determine the maximum value of current or voltage a resistor can handle. In this scenario we can use $P = V^2/R$ to find the maximum voltage V that the resistor can handle. $V = \sqrt{0.25 * 100} = 5 \text{ V}$.


3. Looking at the Resistor P-V Curves graph the power is always positive. Explain in your own words what this means? What happens to the power dissipated in the resistor when you double the voltage? Explain.

Power is always positive in a resistor because it converts electrical energy into heat, regardless of current direction. Resistors can only dissipate energy, not generate it.


Doubling the voltage across a resistor increases the power dissipation by a factor of four, as power ($P=V^2/R$) is proportional to the square of the voltage.



Resistor I-V Characteristic Plot



Current (mA) VS Voltage (V) For 470 ohm

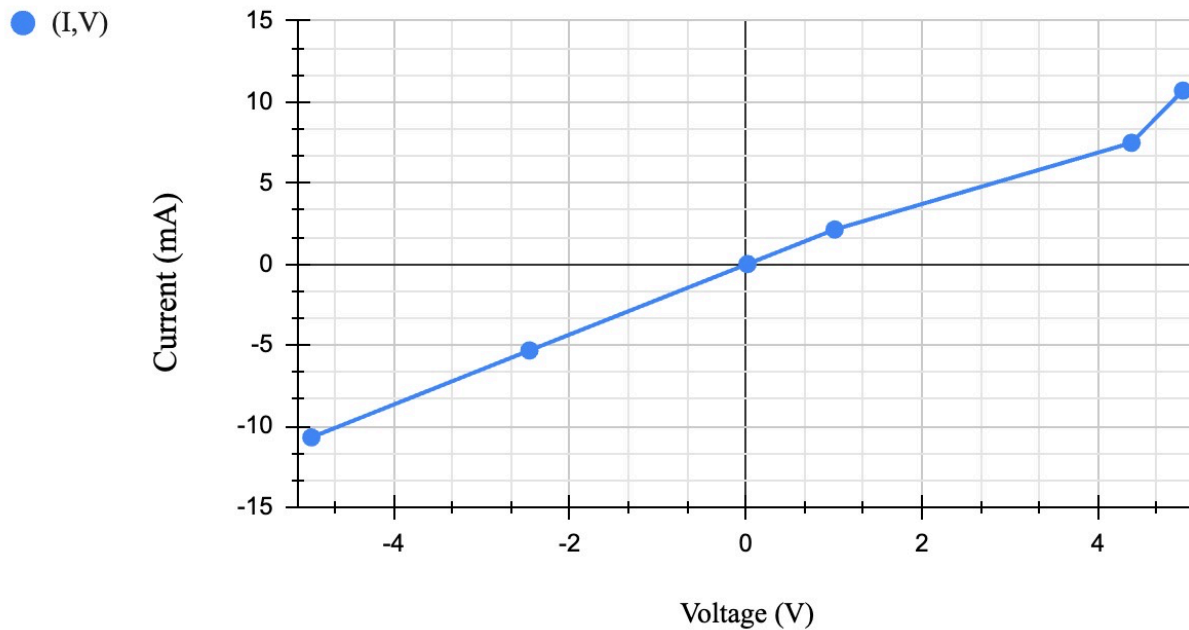

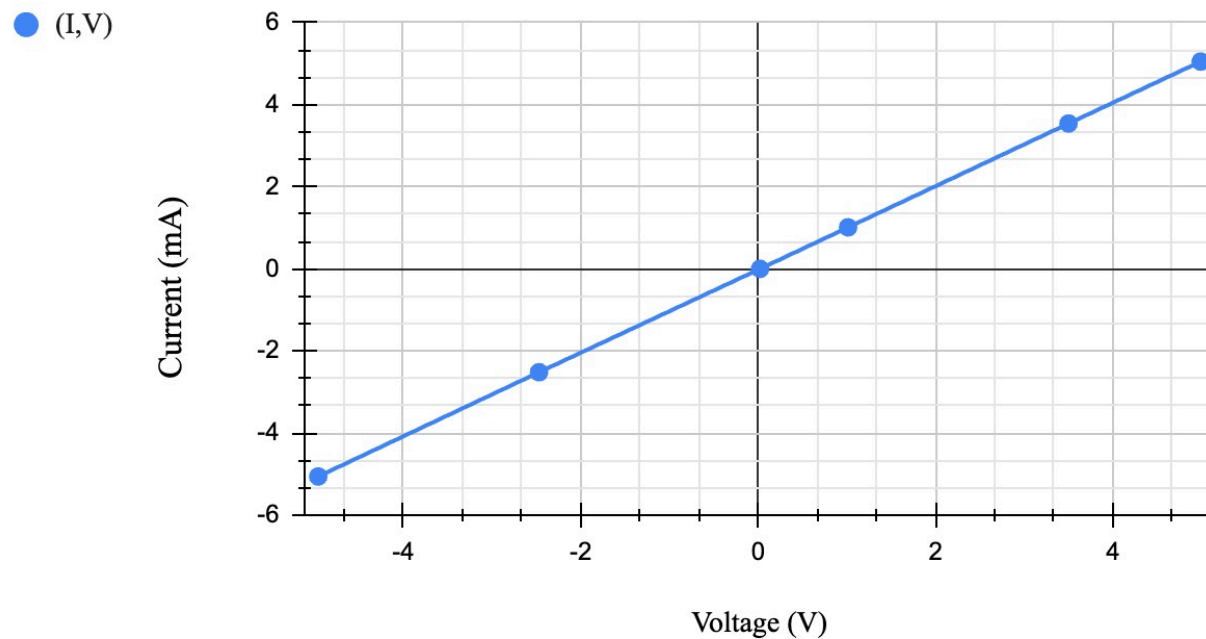Current (mA) VS Voltage (V) For 1.0 k ohm




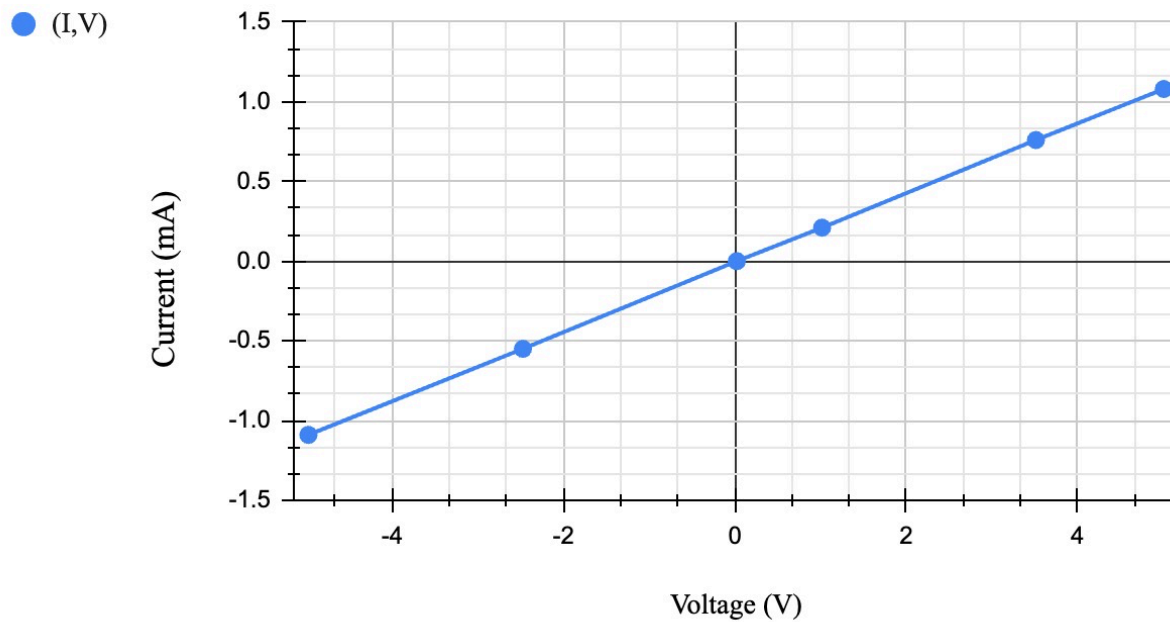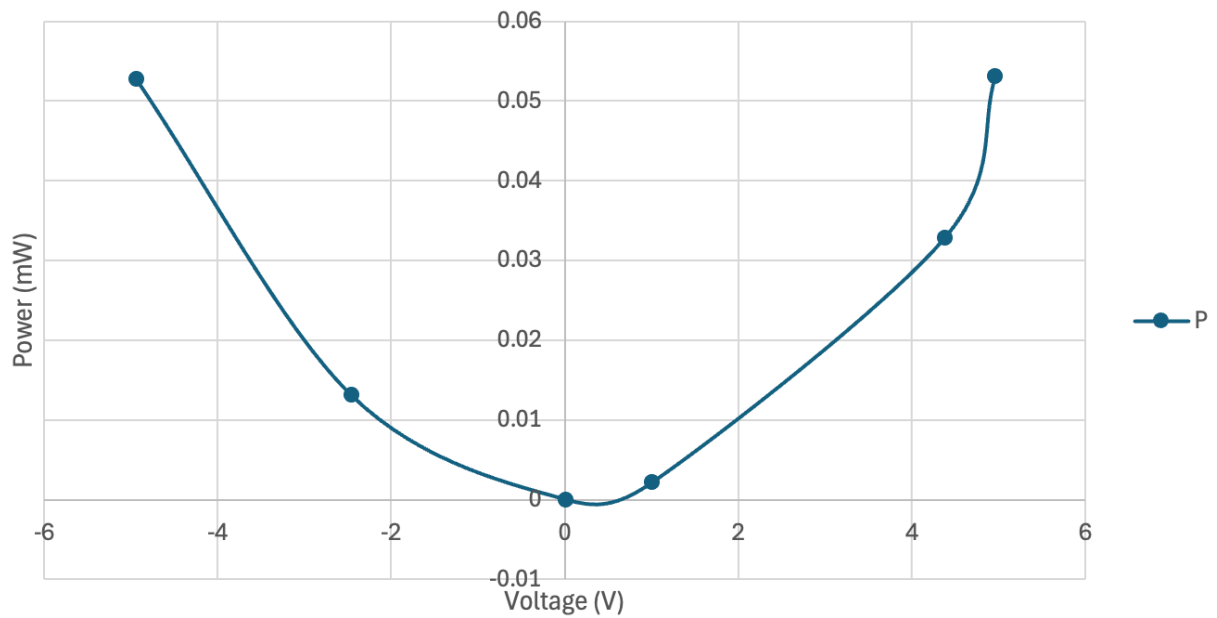Current (mA) VS Voltage (V) For 4.7 k ohm**Resistor P-V Characteristic Plot**Power vs Voltage graph for 470 Ω resistor

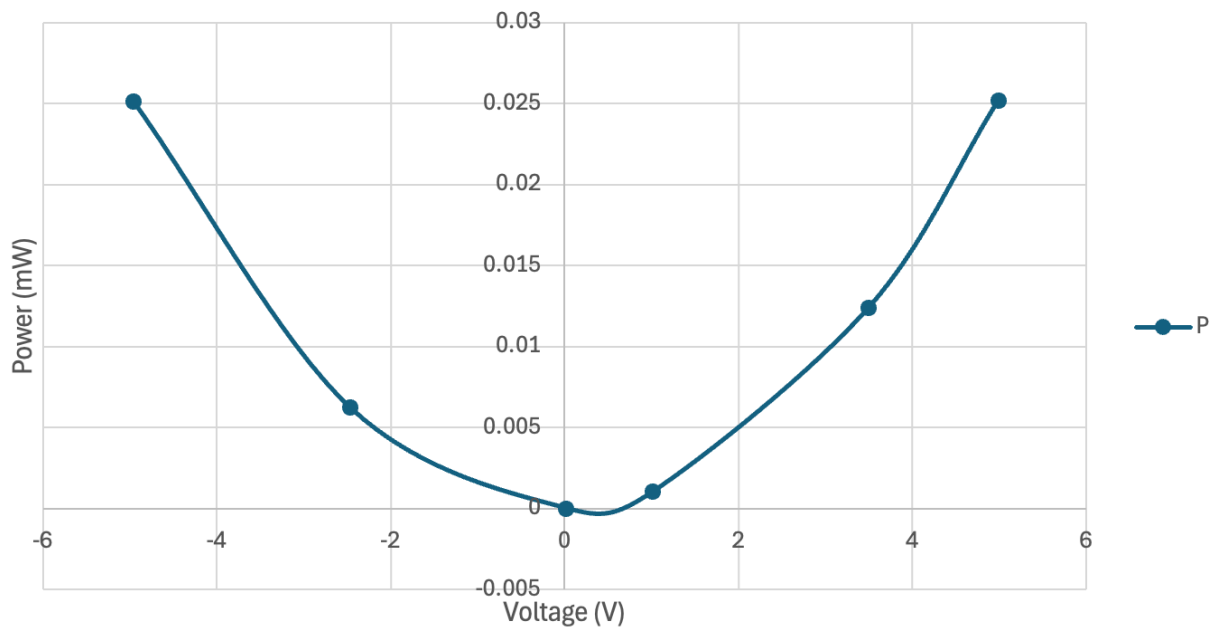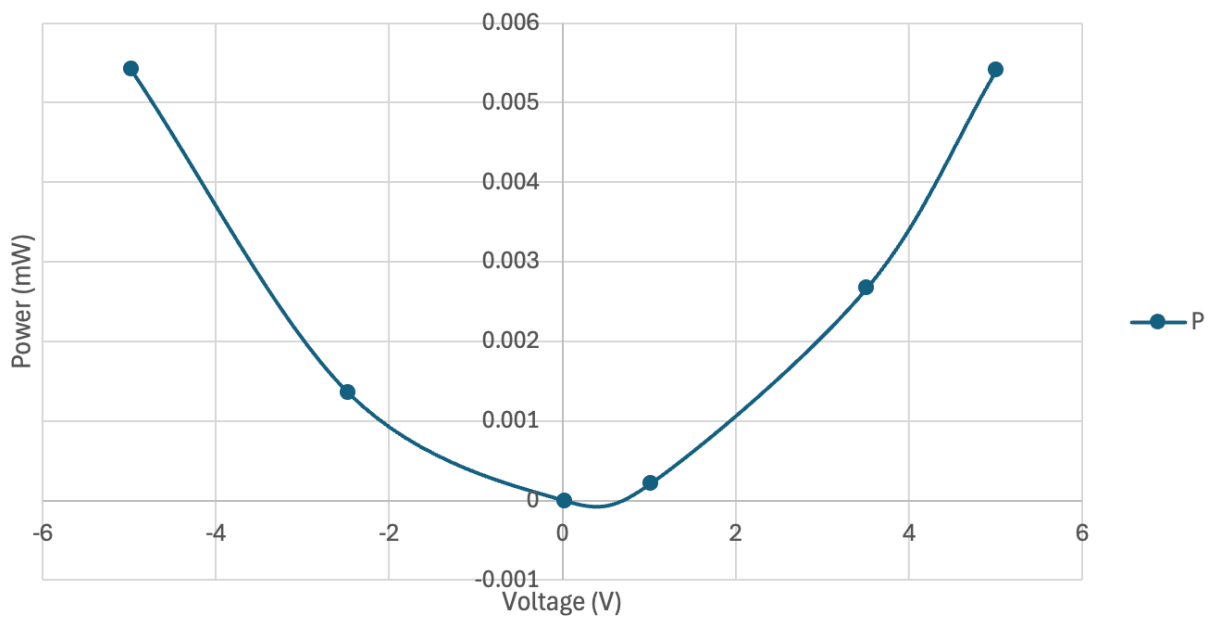
Power vs Voltage graph for 1 k Ω resistorPower vs Voltage graph for 4.7 k Ω resistor


Voltage Divider ($R_1 = 470\Omega$) – Voltage Plot

Voltage Source against Resistance of R_2

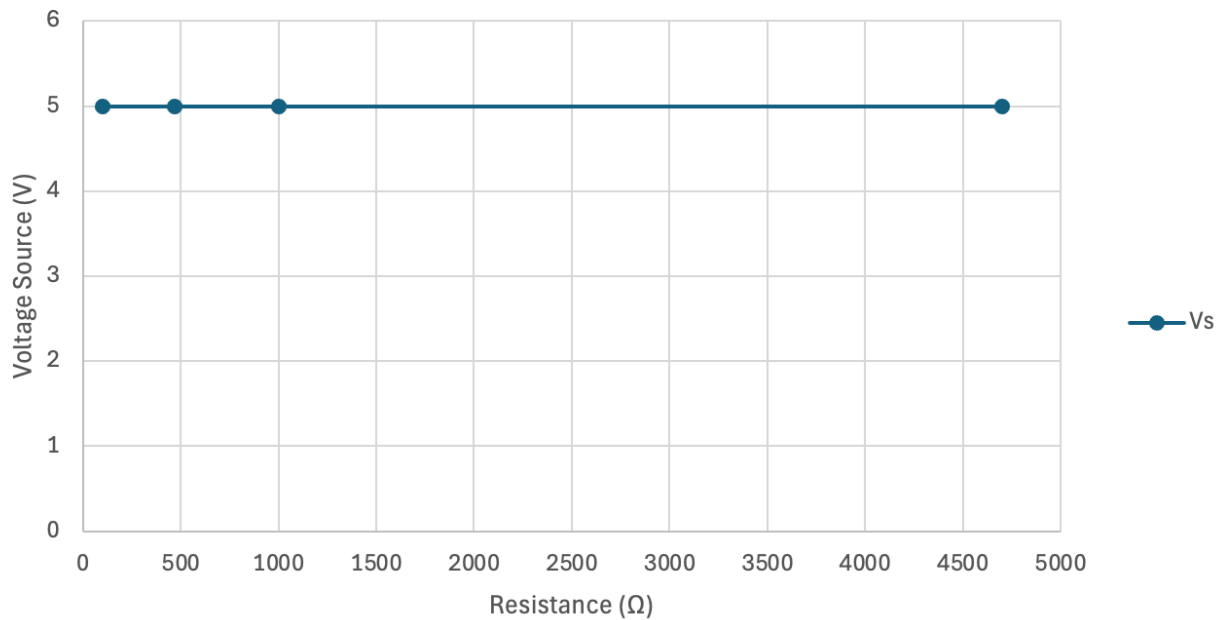

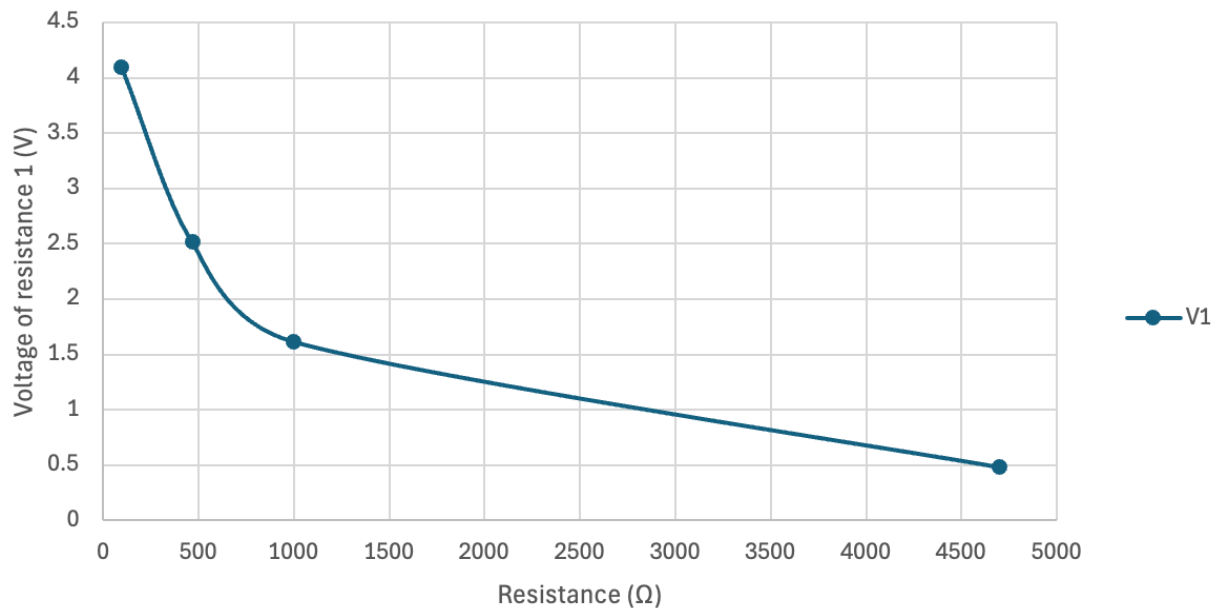
Voltage of Resistance 1 against Resistance value of R_2





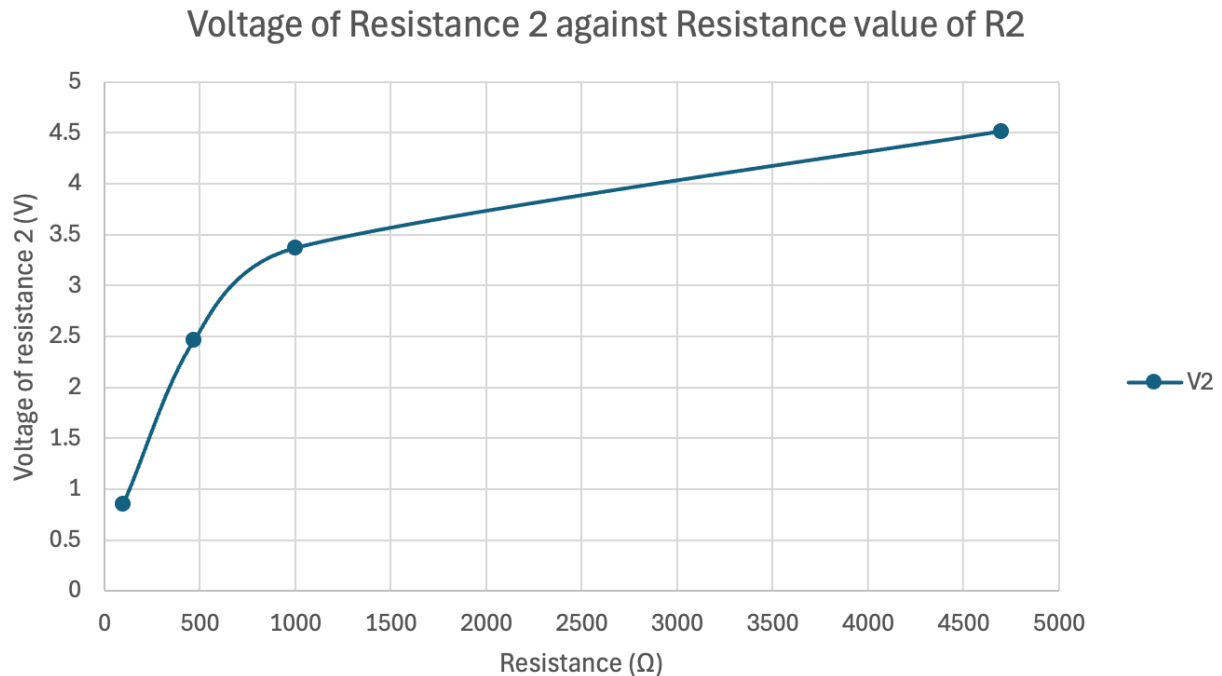


Voltage Divider ($R1 = 470\Omega$) – Power Plot

Power($R1+R2$) (mW) VS. $R2$ (ohm)

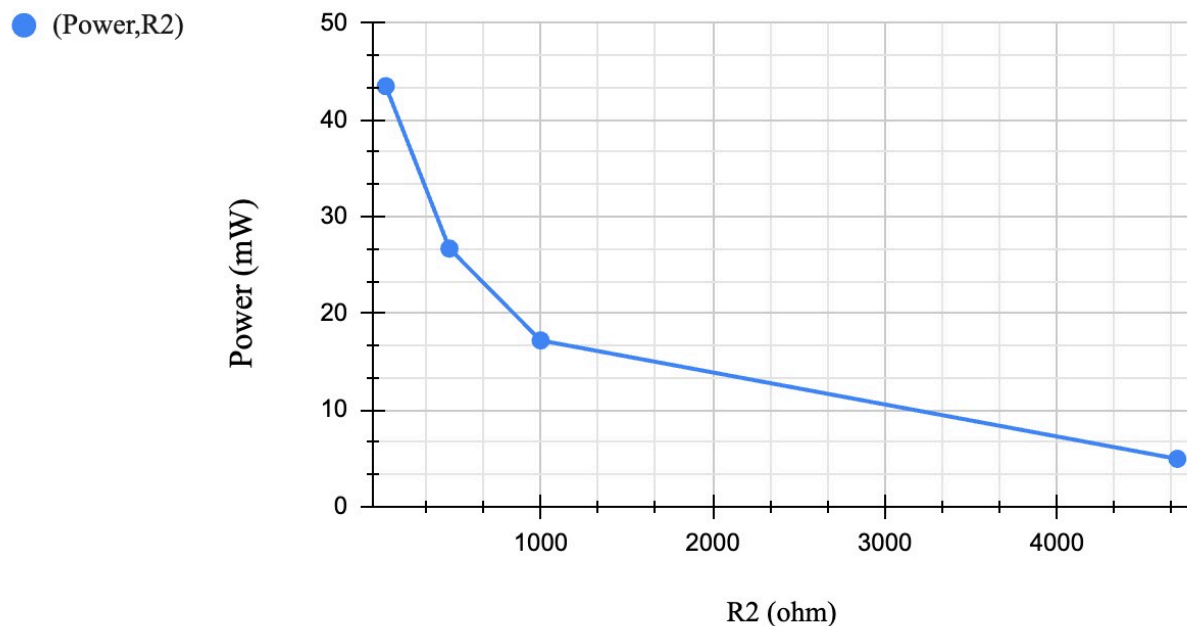


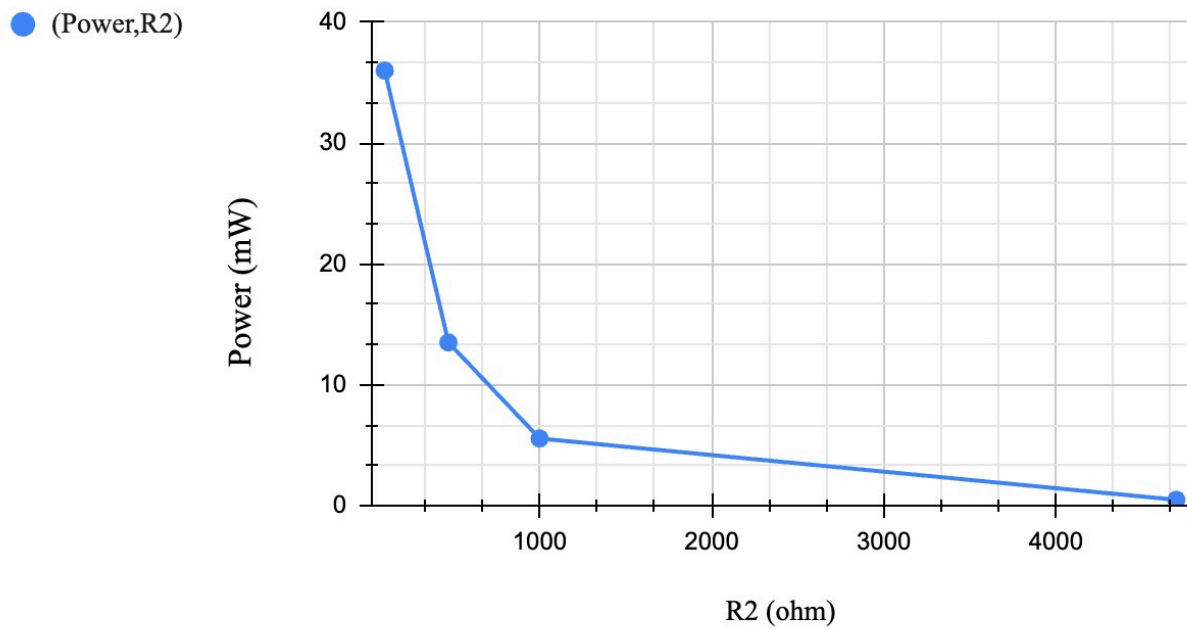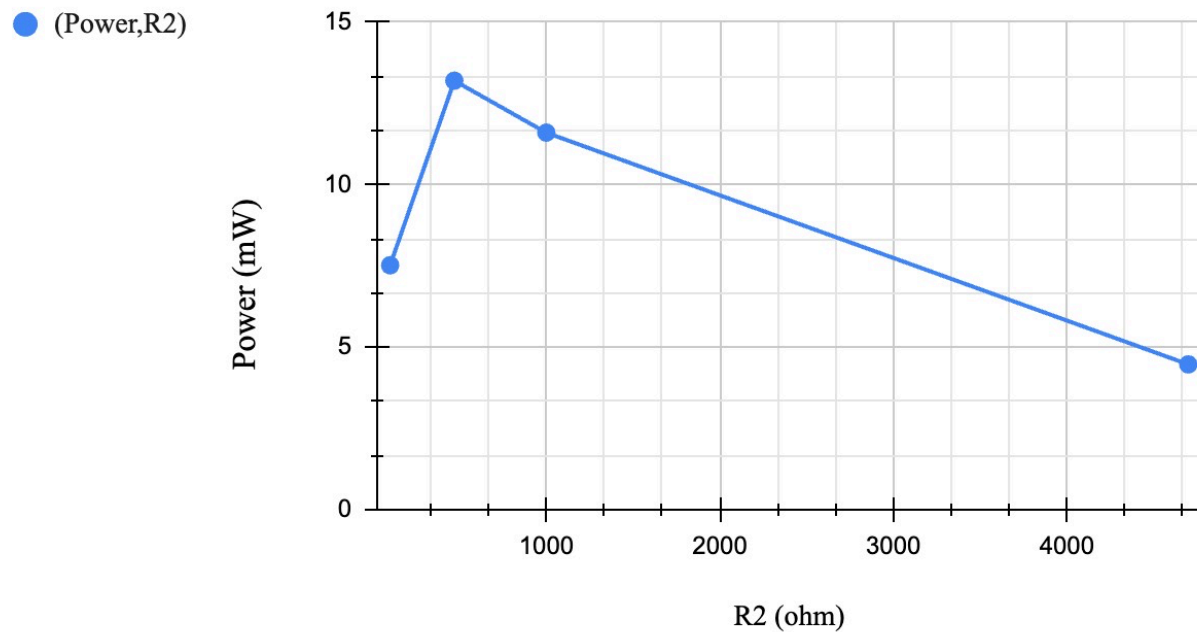
Power (R1) (mW) VS R2 (ohm)**Power (R2) (mW) VS R2 (ohm)****Current Divider ($R1 = 470\Omega$) – Current Plot**

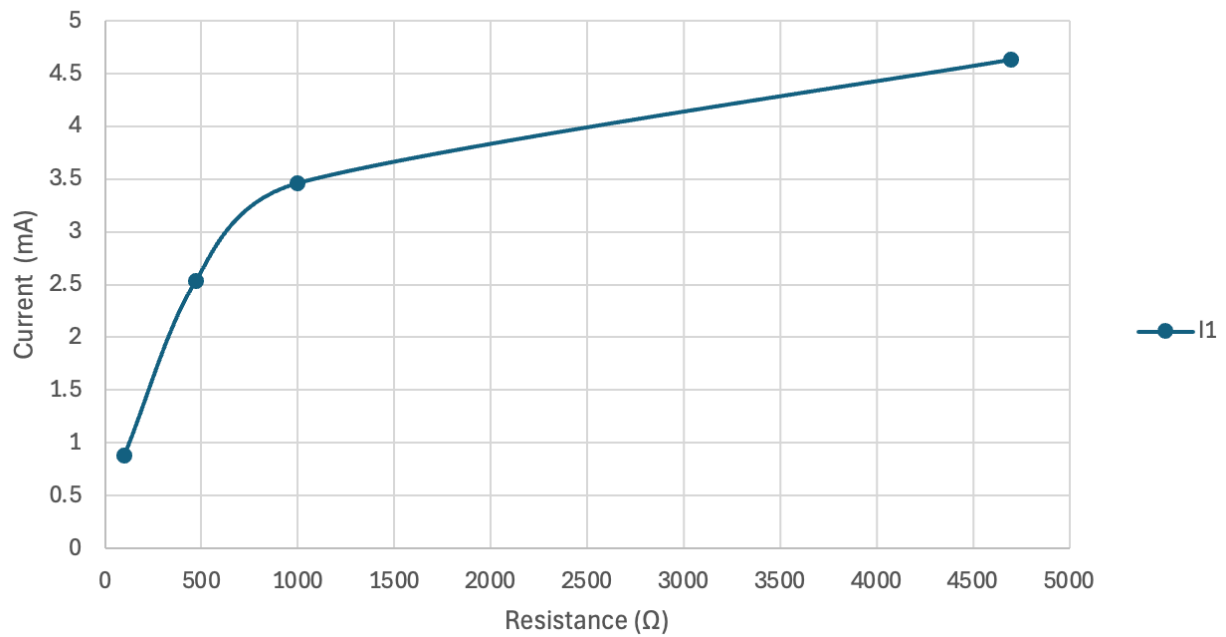Current of R1 against Resistance value of R2



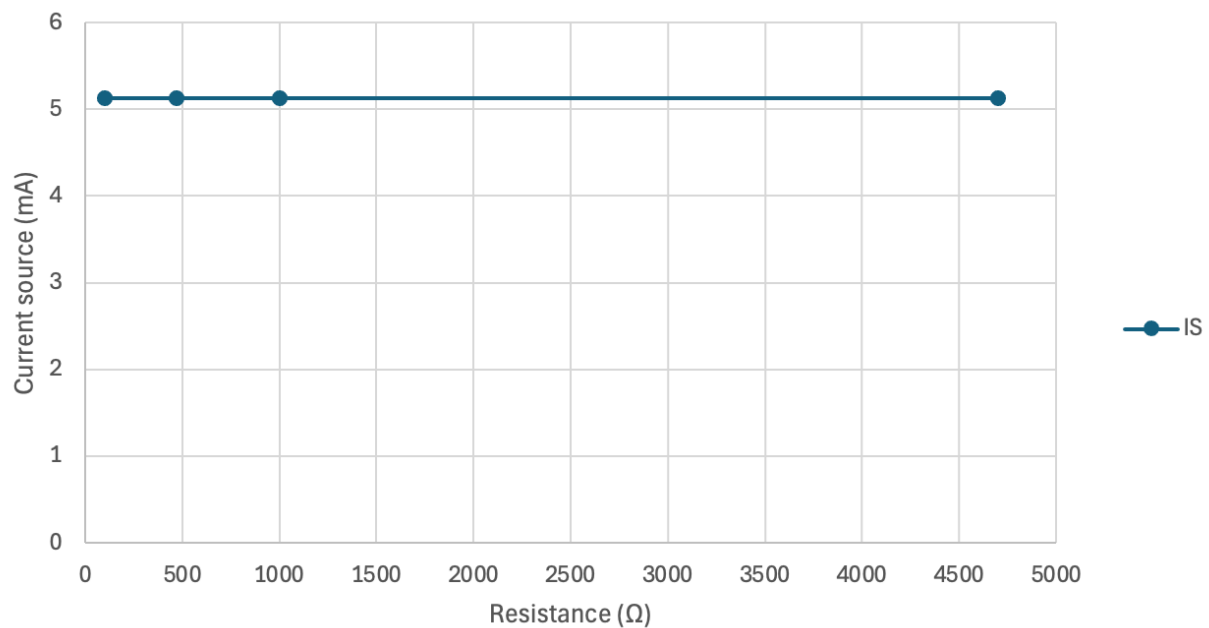
Current source against Resistance value of R2




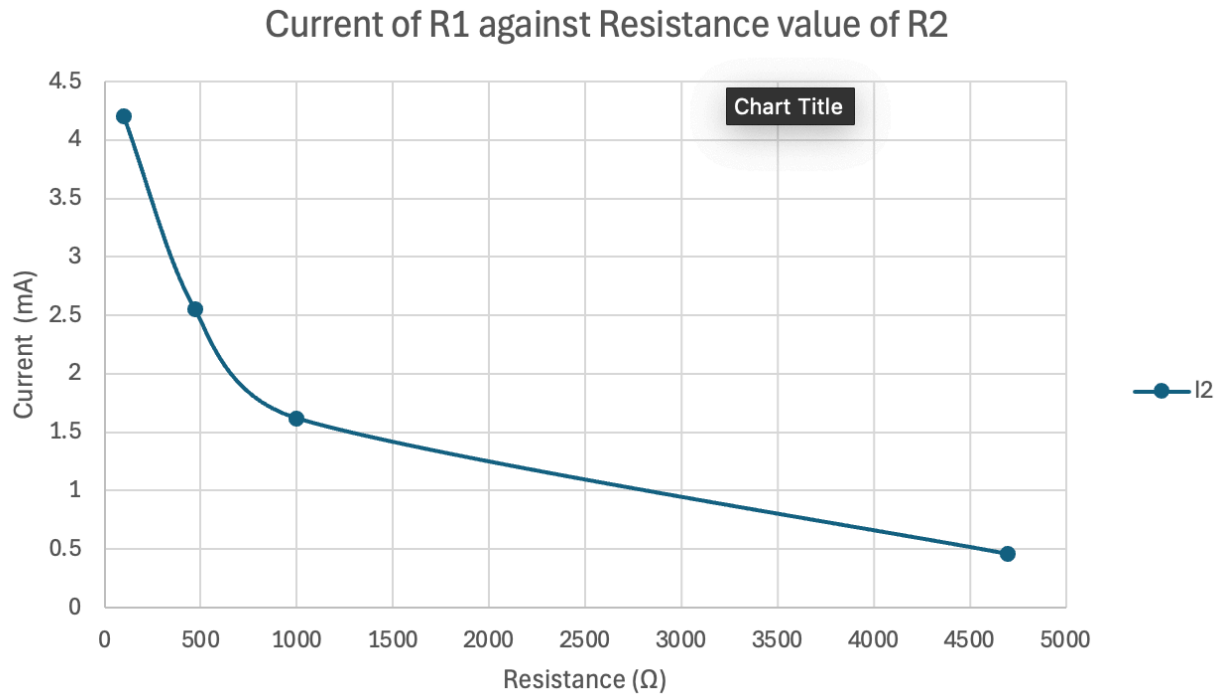

Current Divider ($R_1 = 470\Omega$) – Power Plot

Power (R_2) (mW) VS R_2 (ohm)

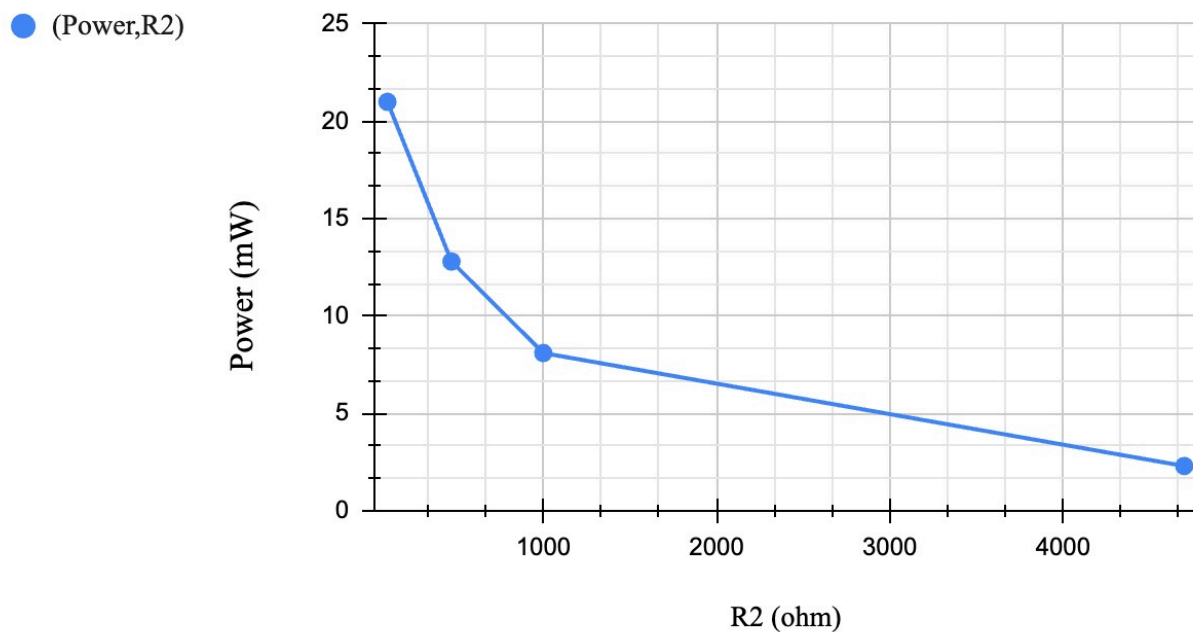

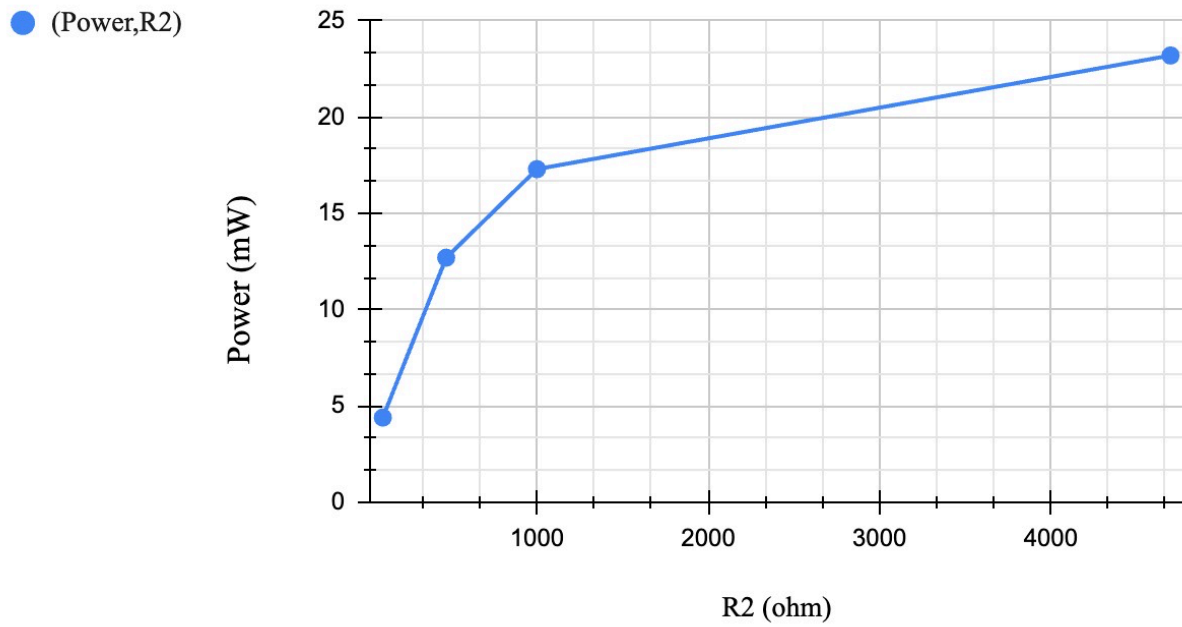Power (R1) (mW) VS R1 (ohm)**Power (R1+R2) (mW) VS R1 (ohm)**