

Lab 2 Results – Circuit Theorems

ECE202: Fundamentals of Electrical Engineering

Name	Student ID	CCID
Misbah Ahmed Nauman	1830574	misbahah
Muhammad Abdur Rab Siddiqui	1804733	msiddiq6

2.1 Delta-Wye Transformations

Wye						
	R1(Ω)	R2(Ω)	R3(Ω)	u-v(Ω)	v-w(Ω)	w-u(Ω)
Measured	215.7	458.6	319.5	673	777	535.2
Calculated	209.5	461.4	314.7	978	1469	667
Delta						
	Ra(Ω)	Rb(Ω)	Rc(Ω)	x-y(Ω)	y-z(Ω)	z-x(Ω)
Measured	1469	667	978	672	777	525.6
Calculated	1457.4	685.5	983.9	983.9	1457.4	685.5

2.2 The Test Circuit

R_load	Vb	Va	V_R1	V_R2	V_load	Ib	Ia	I_load
(Ω)	(V)	(V)	(V)	(V)	(V)	(mA)	(mA)	(mA)
100	3.2538	5.0103	4.3062	2.9795	0.681	3.83	2.91	6.74
220	3.2578	5.0102	3.76	2.04	1.23	3.03	2.94	5.58
470	3.259	5.0107	3.08	1.36	1.9162	2.02	2.56	4.11
1000	3.2625	5.0106	2.388	0.6717	2.6097	1.01	2.02	2.62
2200	3.2656	5.0113	1.839	0.124	3.155	0.19	1.36	1.44

2.3 The Test Circuit

2.3.1 V_b Acting Alone

R _{load}	V _b	V _a	V _{R1}	V _{R2}	V _{load}	I _b	I _a	I _{load}
(Ω)	(V)	(V)	(V)	(V)	(V)	(mA)	(mA)	(mA)
100	3.2545	0.0125	0.4116	2.8813	0.3822	4.25	0.26	3.98
220	3.2538	0.0133	0.733	2.5602	0.706	3.78	0.48	3.29
470	3.2583	0.0126	1.1355	2.1601	1.1162	3.17	0.76	2.41
1000	3.2589	0.0124	1.5419	1.7527	1.5175	2.58	1.03	1.54
2200	3.2600	0.0128	1.8662	1.4318	1.839	2.10	1.25	0.85

2.3.2 V_a Acting Alone

R _{load}	V _b	V _a	V _{R1}	V _{R2}	V _{load}	I _b	I _a	I _{load}
(Ω)	(V)	(V)	(V)	(V)	(V)	(mA)	(mA)	(mA)
100	0.009	5.0108	4.7344	0.2677	0.289	0.40	3.18	2.75
220	0.0108	5.0113	4.5101	0.4912	0.513	0.73	3.03	2.28
470	0.0095	5.011	4.2292	0.772	0.794	1.14	2.84	1.68
1000	0.0071	5.0109	3.947	1.0531	1.077	1.57	2.65	1.07
2200	0.0083	5.0104	3.7226	1.2752	1.3013	1.90	2.50	0.59

Superposition (V_b Acting Alone + V_a Acting Alone)

R _{load}	V _b	V _a	V _{R1}	V _{R2}	V _{load}	I _b	I _a	I _{load}
(Ω)	(V)	(V)	(V)	(V)	(V)	(mA)	(mA)	(mA)
100	3.2635	5.0233	5.146	3.149	0.6712	4.65	3.44	6.73
220	3.2646	5.0246	5.2431	3.0514	1.219	4.51	3.51	5.57
470	3.2678	5.0236	5.3647	2.9321	1.9102	4.31	3.6	4.09
1000	3.266	5.0233	5.4889	2.8058	2.5945	4.15	3.68	2.61

2200	3.2683	5.0232	5.5888	2.707	3.1403	4	3.75	1.44
------	--------	--------	--------	-------	--------	---	------	------

2.4 Thevenin/Norton

2.4.1 Equivalent Parameters

V _{th}	(V)	3.82
I _{norton}	(mA)	8.2
R _{th} /R _{norton}	(Ω)	460.7

2.4.2 Thevenin Circuit

V _{th} (measured)	(V)	3.8345
R _{th} (measured)	(Ω)	458.7

R _{load}	V _{load}	I _{load}	P _{source}	P _{load}	η
(Ω)	(V)	(mA)	(mW)	(mW)	(%)
100	0.6512	6.73	32.05	4.38	13.7
220	1.195	5.56	32.05	6.64	20.7
470	1.8876	4.09	32.05	7.72	24.1
1000	2.5722	2.63	32.05	6.76	21.9
2200	3.1256	1.45	32.05	4.53	14.1


1) Show your work for finding P_{source}, P_{load} and η for the case of R_{load} at 220 Ω for Thevenin Circuit.

$$P_{\text{load}} = [V_{\text{th}} (\text{measured})]^2 / R_{\text{th}} (\text{measured}) = (3.8345 \text{ V})^2 / 458.7 \text{ } \Omega = 32.05 \text{ mW}$$

$$P_{\text{load}} = V_{\text{load}} * I_{\text{load}} = 1.195 \text{ V} * 5.56 \text{ mA} = 6.64 \text{ mW}$$

$$\eta = (P_{\text{load}} / P_{\text{source}}) * 100\% = (6.64 / 32.05) * 100\% = 20.7 \%$$

2.4.3 Norton Circuit

 I_norton (measured)	(mA)	8.64
R_norton (measured)	(Ω)	458.7

R_load	V_load	I_load	P_source	P_load	η
(Ω)	(V)	(mA)	(mW)	(mW)	(%)
100	0.68	7.08	34.2	4.81	14.1
220	1.25	5.83	34.2	7.29	21.3
470	1.975	4.27	34.2	8.43	24.6
1000	2.683	2.74	34.2	7.35	21.5
2200	3.252	1.51	34.2	4.91	14.4

2) What are the three different strategies described in the lab procedures for measuring R_{th}/R_{norton} .

Strategy 1: Calculate the Thevenin/Norton resistance by dividing the Thevenin-equivalent voltage by the Norton-equivalent current

Strategy 2: Adjust the load resistance R_{load} until the voltage across it equals half of the Thevenin-equivalent voltage. At this point, R_{load} is equal to both R_{TH} and R_{NORTON} .

Strategy 3: Replace all sources with their internal resistances (shorting voltage sources and opening current sources) and measure the resistance at the terminals.

3) Looking at both the Thevenin circuit and Norton circuit plot, what is the value of R_{load} which gives the maximum power? What is the efficiency at this operating point? Is this efficiency maximum?

In both Thevenin circuit and Norton circuit plot $R_{\text{load}} = 470 \, \Omega$ gives the maximum power. For Thevenin circuit efficiency is 24.1 % and for Norton circuit efficiency is 24.6% both of which are efficiency maximum respectively.

4) Comparing the Thevenin I-V Characteristic Curve to the Norton Characteristic curve, would you say that these circuits perform equivalently?

Yes, the Thevenin and Norton circuits perform equivalently in terms of their electrical characteristics. Both are two different ways of representing the same circuit, and their I-V characteristic curves are similar as can be seen by the plots on next few pages. This is because the Thevenin circuit uses a voltage source in series with a resistor, while the Norton circuit uses a current source in parallel with a resistor. When you convert between the two, the voltage and current relationships are preserved, which is why they show similar behavior.

Load I-V Characteristic Plot

The following pages have been left for you to include the plots that you are required to create as part of your post-lab.


To create your plots you can use whichever software you would like (Excel, Matlab, etc), export your plot as an image and import it into your Lab 2 - Results sheet in the appropriate place.

Your plots should include:

- A Plot title
- Label your axes and show what unit of measure is used.
- Include a marking for your data-points.
- Include a line between your data-points in the same series.
- Include a legend.
- Make sure your scales are appropriate and visible.

For each of these 3 circuits: The Test Circuit, Thevenin Circuit and Norton Circuit plot the load current vs. load voltage on the same plot.

I load (mA) VS. V load (V)

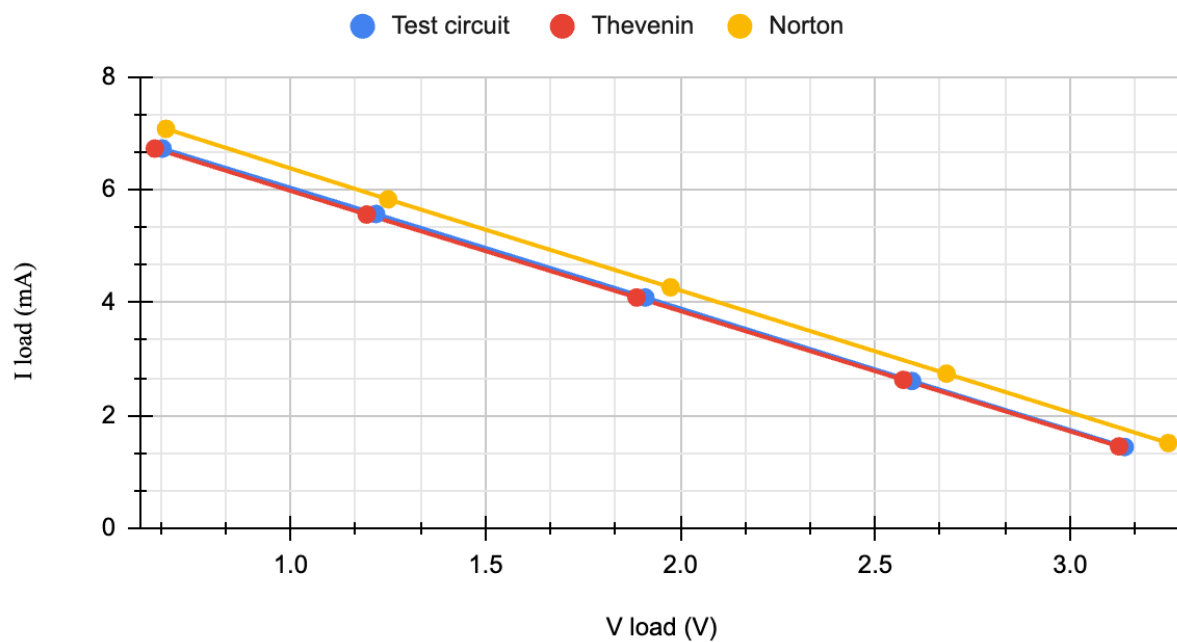


Thevenin Circuit Plot

For your Thevenin Circuit results:

Plot the load power vs. load resistance as one series and the circuit efficiency vs. load resistance (R_2) as a second series using a secondary y-axis scale.

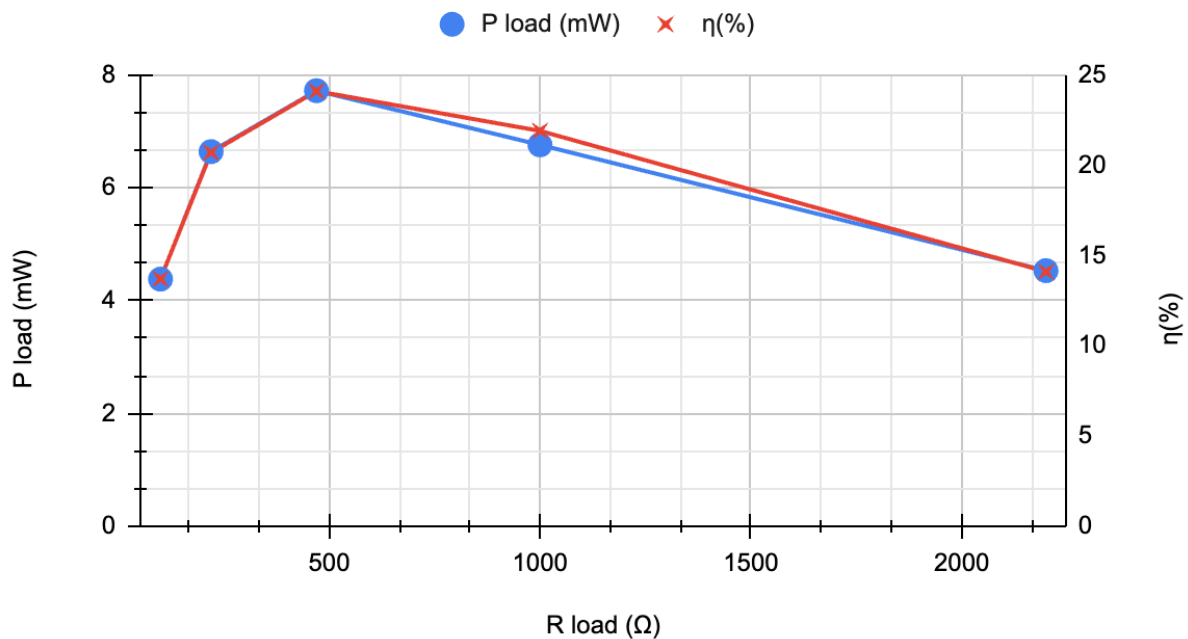P load (mW) vs. R load (Ω) and $\eta(\%)$ vs. R load (Ω)



Norton Circuit Plot

For your Norton Circuit results:

Plot the load power vs. load resistance as one series and the circuit efficiency vs. load resistance (R_L) as a second series using a secondary y-axis scale.

P load (mW) vs. R load (Ω) and $\eta(\%)$ vs. R load (Ω)

