

Lab 2 – Circuit Theorems

ECE202-Electrical Circuits-I

Electrical and Computer Engineering - University of Alberta

1. Objectives

In this second lab session, you will continue to use the common electrical tools & components used for circuits in your Lab kit and use them to experimentally test and confirm the validity of circuit theorems that are taught in the lectures. The objectives are as follows:

1. Introduce the following devices:
 - 2nd DC Voltage Source - (WaveGen as a DC Source)
2. Introduce the following concepts:
 - Delta-Wye Transformations
 - Superposition
 - Thevenin's Theorem
 - Norton's Theorem
 - Thevenin-Norton Equivalency
 - Maximum Power Transfer

1.1 Instructions for ECE202 lab:

- Labs are typically completed in groups of two, so please try to pair up before coming to the lab. If you can't find a partner we will either pair you up in the lab or you may also be permitted to work by yourself. Only one lab report is required per group if you are working in a group, but please make sure to include the names, CCIDs, and student IDs of both students on the result sheet. Information regarding the due date of Lab 2 report submission is available on eClass lab schedule.
- Make sure you have either an electronic device with you where you can access this lab manual or print out the Lab 2 Manual before coming to your lab session.
- Lab 2 results sheet (available on lab eClass) to record your measurements during the lab session. **Everything in light blue on the results sheet is part of the post lab calculations.**

1.2 Equipment Required

- A Computer with [Waveforms](#) installed
- [Analog Discovery 2](#)
- [Breadboard Breakout](#) for the Analog Discovery 2 with a Ribbon Cable
- A USB A to Micro-B cable
- Digital multimeter
- MB102 breadboard
- DC Current Source LM234Z ([Data sheet of LM234Z](#))
- 1k Ω pot
- Jumper wires
- The following resistors (1/4 watt or 0.6watt, 1% or 5%)
 - 3.6 Ω
 - 4.7 Ω
 - 100 Ω
 - 220 Ω
 - two 470 Ω
 - 680 Ω
 - 1k Ω
 - 1.5k Ω
 - 2.2k Ω

1.3 Background

- [Delta-Wye Transformations](#)
- [Superposition Theorem](#)
- [Thevenin's Theorem](#)
- [Norton's Theorem](#)
- [Thevenin-Norton Equivalencies](#)
- [Maximum Power Transfer Theorem](#)

(Please refer to the textbook to understand the above mentioned topics, website links provided here are just for reference.)

2. Procedures

2.1 Delta-Wye Transformations

Delta → Wye transformation

Equations for transforming a Delta network into a Wye network,

$$R1 = \frac{Rb Rc}{Ra + Rb + Rc}$$

$$R2 = \frac{Ra Rc}{Ra + Rb + Rc}$$

$$R3 = \frac{Ra Rb}{Ra + Rb + Rc}$$

Note: Transforming from Delta to Wye introduces one additional node.

Wye → Delta transformation

Equations for transforming a Wye network into a Delta network,


$$Ra = \frac{R1 R2 + R2 R3 + R3 R1}{R1}$$

$$Rb = \frac{R1 R2 + R2 R3 + R3 R1}{R2}$$

$$Rc = \frac{R1 R2 + R2 R3 + R3 R1}{R3}$$

Note: Transforming from Delta to Wye introduces one additional node.


1. Measure the resistance values of a wye connected resistor network shown below.

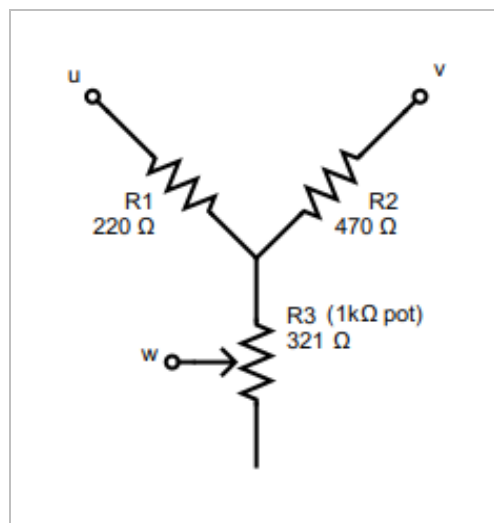

Circuit 1: Wye test circuit

- a. Connect the circuit above using the following:
 - Connect 220Ω, 470Ω resistors and the 1kΩ potentiometer as a wye on the breadboard.

- Use the digital multimeter (DMM) to measure and record the resistance of R1, R2 and R3. When measuring R3, adjust the potentiometer knob until a resistance of $\sim 321\Omega$ is achieved between the center pin and the pin that connects to the other two resistors.
 - b. Use the DMM to now measure the resistance between the terminals labeled u-v, v-w and w-u and record your measurements on the results sheet.
2. Measure the resistance values of the delta connected resistor network that is the approximate equivalent of the wye connected network from the previous step.

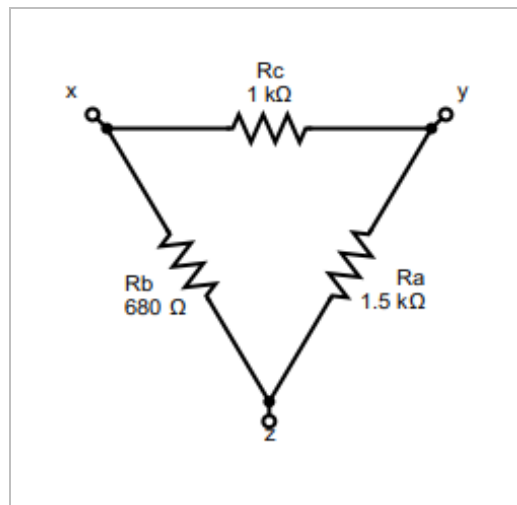

Circuit 2: Delta test circuit

- a. Before connecting the circuit above, use the DMM as an ohmmeter to measure the resistors you are going to use for Ra, Rb and Rc and record those resistances on the results sheet.
- b. Connect the resistors Ra, Rb and Rc that you measured above as a delta connected resistor network on the breadboard.
- c. Use the DMM to now measure the resistance between the terminals labeled x-y, y-z and z-x and record your measurements on the results sheet.

2.2 The Test Circuit

3. Use the Test Circuit below as a starting point to accomplish 2 things: First to test if the Superposition Theorem is valid, then to see if Thevenin and Norton theorems are valid.


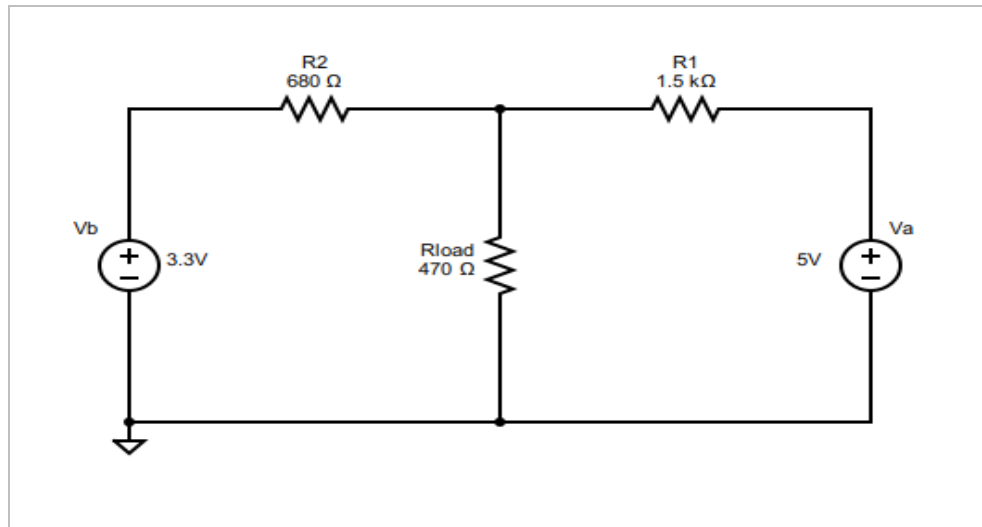


Figure 1: The test circuit

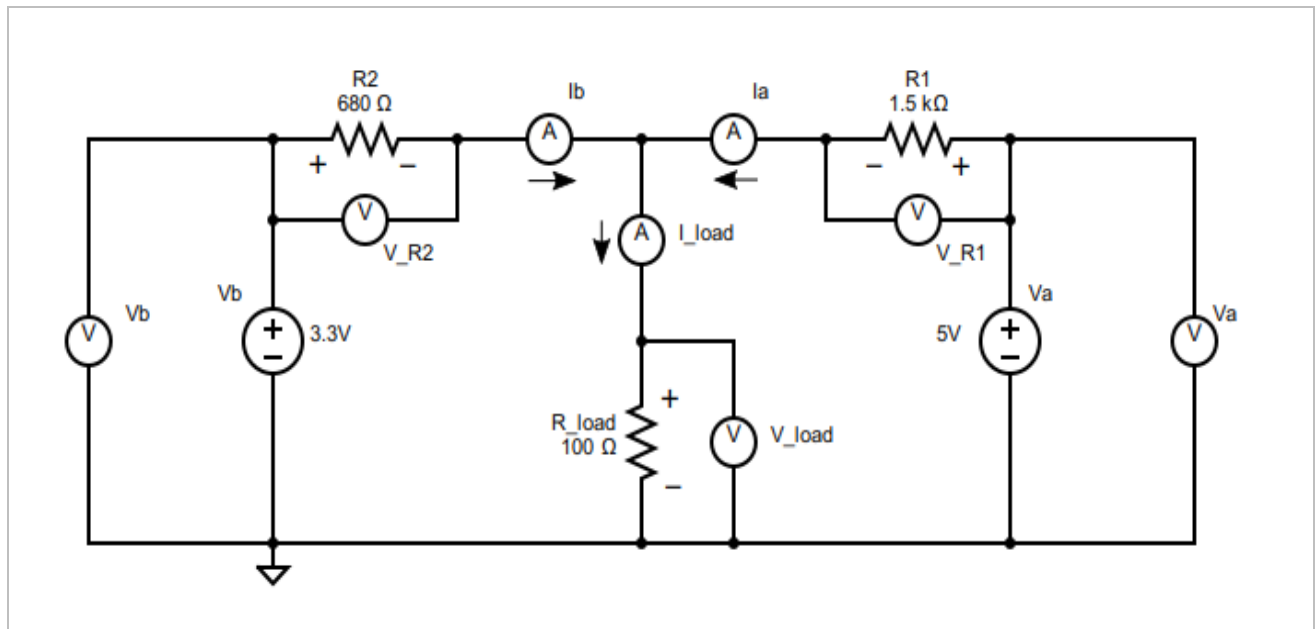

Circuit 3: The test circuit (shown with meter placement)

Note: Above test circuit shows all of the meter placement, however you have an only one DMM to measure current so you cannot take all the current readings at the same time.

a. Connect the circuit above using the following:

- Use a 1.5kΩ resistor for R1, a 680Ω resistor for R2. For R_load start with a 100Ω resistor, you will switch out this resistor a few times for another value when required.
- Use the positive DC voltage source from the Analog Discovery 2 as Va (V+ and Gnd). Set it to +5V but don't enable it yet.

- Use the 'Wavegen' channel 1 (W1) as a second positive DC voltage source from the Analog Discovery 2 for V_b (W1 and Gnd). Do not press Run yet but you can configure it with following parameters:
 - Type = 'DC'
 - Offset = '3.3V'
- Use Voltmeter channels 1 (1+ and 1-) and 2 (2+ and 2-) from the Analog Discovery to measure all the required voltages (V_a , V_b , V_{R1} , V_{R2} and V_{load}). You will have to move the opposite end of the 2 jumper wires that connect to the channel inputs (i.e. 1+ and 1-) across the device you would like to measure one at a time.

Note: Voltage Polarity

As you will measure the voltage across the same location multiple times as the circuit changes slightly as you go through this laboratory exercise, you need to keep the measured polarities constant.

You can see in the circuit schematic above that each voltage that needs to be measured is represented as a voltmeter which also has a + and - near each terminal indicating which way you should make your measurement.

To be consistent, always connect the voltmeter + input (i.e. 1+ or 2+ on the Analog Discovery 2) to the side with the + symbol on the schematic. Do the same for the -.

- Use the DMM as a milliammeter to measure all of the required currents (I_b , I_a and I_{load}). You will have to move the milliammeter to the appropriate place in the circuit to make the measurements one at a time.

Note: Moving the milliammeter

If you want to place the DMM into the circuit somewhere you need to break the existing circuit so you can insert the milliammeter.

If the DMM is a part of the circuit and you remove it you will create an open circuit where the milliammeter once was, you will need to replace the DMM with a shorting jumper wire to maintain the circuit.

Note: Current Polarity

As you will measure the current in the same location multiple times as the circuit changes slightly as you go through this laboratory exercise, you need to keep the measured polarities constant.

You can see in the circuit schematic above that each current that needs to be measured is represented by an ammeter with an arrow beside it. The arrow shows the polarity in which the measurement should be made.

To be consistent, always connect the black lead of the DMM to the side with the arrow-head and the red lead to the opposite side. When connected this way the ammeter will give you a positive current when the current is traveling in the same direction of the arrow and a negative current when traveling in the direction opposite the arrow.

b. The circuit should look something like this when completed.

- Channel 1 is currently measuring V_{R1}
- Channel 2 is currently measuring V_{R2}
- The DMM is currently measuring I_b

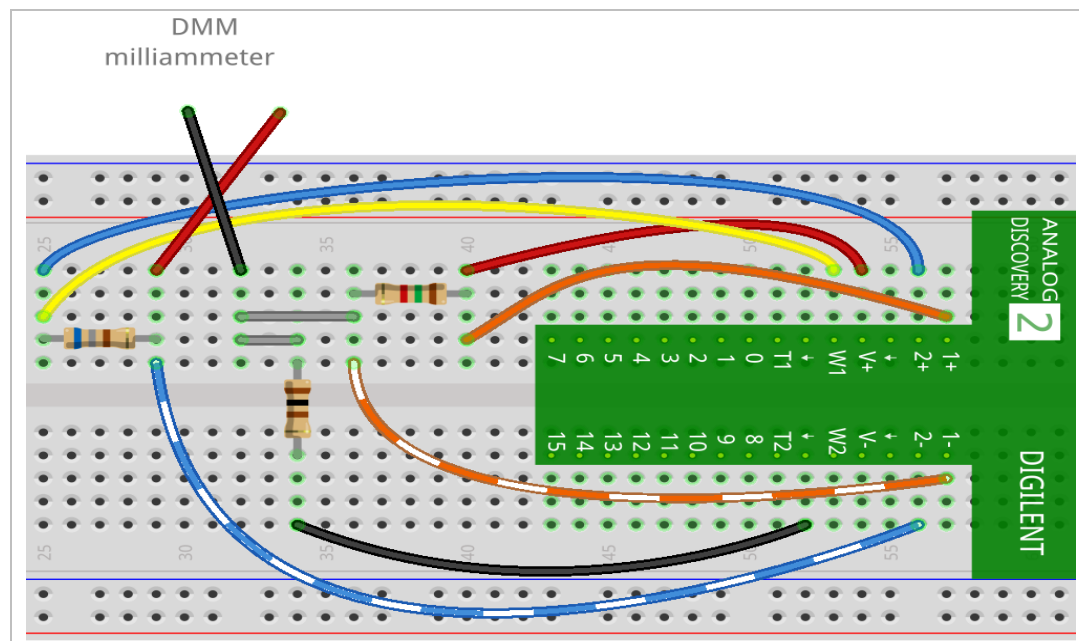


Figure 2: The test circuit shown on breadboard

- c. Activate both DC voltage sources in Waveforms by enabling the required settings.
- On the 'Supplies' window select the appropriate enable buttons.
 - On the 'Wavegen' window click on the run button, this should also check the checkbox automatically.



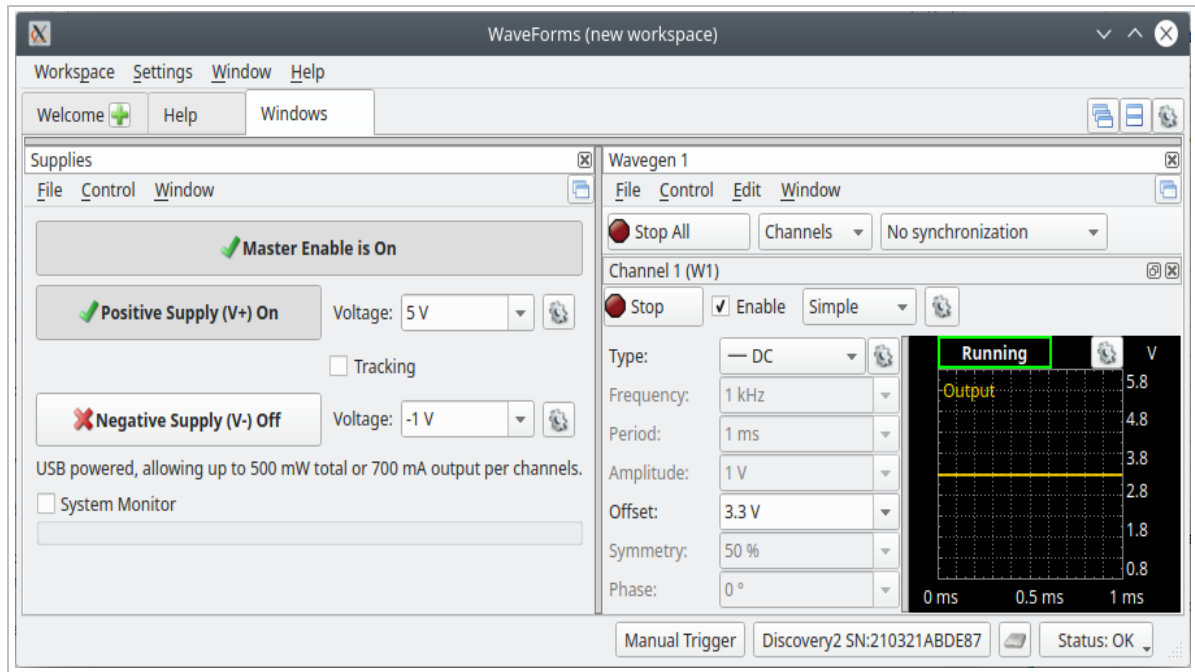


Figure 3: Using DC supply on both the Supplies screen and Wavegen screen


- d. Measure all voltages (V_a , V_b , V_{load} , V_{R1} and V_{R2}) and all of the currents (I_a , I_b and I_{load}) and record it on your results sheet for this value of R_{load} (100Ω). In order to measure current I_a , I_b and I_{load} you must use a multimeter as a milliammeter and connect it to appropriate place in the circuit. You can use below given circuits 3a, 3b and 3c for your reference when measuring I_{load} , I_a and I_b respectively.
- e. Change the load resistor (R_{load}) to different values one at a time (220Ω , 470Ω , $1.0k\Omega$ and $2.2k\Omega$) and make all of the same measurements again for each value making sure to record your measurement on your results sheet.

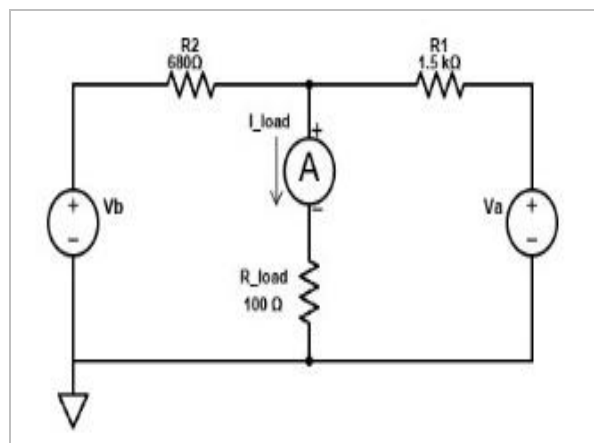

Circuit 3a. Superposition Test circuit (When measuring I_{load})

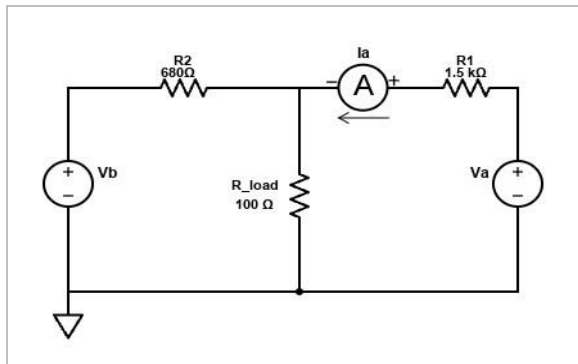

Circuit 3b. Superposition Test circuit
(When measuring I_a)

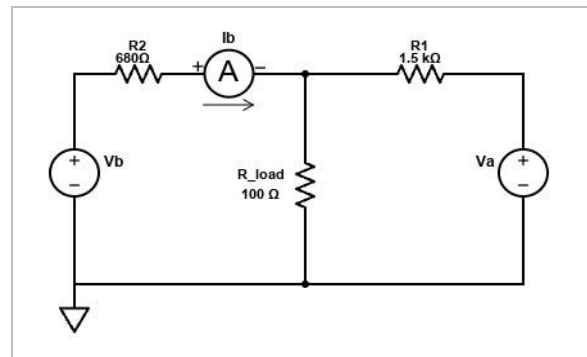

Circuit 3c. Superposition Test circuit
(When measuring I_b)

Note: Another way

Some people may find it easier/quicker to set up the voltmeters and ammeter to each measure a single measurement and then simply swap out the R_{load} resistor to get the measurements for the 5 different R_{load} values. Then move all of the meters to a new location and again get the measurements for different R_{load} values. Repeat until you have recorded all of the measurements required for The Test Circuit.

- f. After the completion of this section just turn off the voltage sources (V_b and V_a) as you will continue to use this circuit in the Superposition section.

2.3 Superposition

Superposition Theorem

For a linear system the response (voltage or current) in any branch of a bilateral linear circuit having more than one independent source equals the algebraic sum of the responses caused by each independent source acting alone when all the other independent sources are replaced by their internal resistances.

2.3.1 V_b Acting Alone

4. To test the superposition theorem you need to test the influence of each source on the circuit independently. Configure the Test Circuit from the previous step to see how the circuit responds when only supplied by V_b .


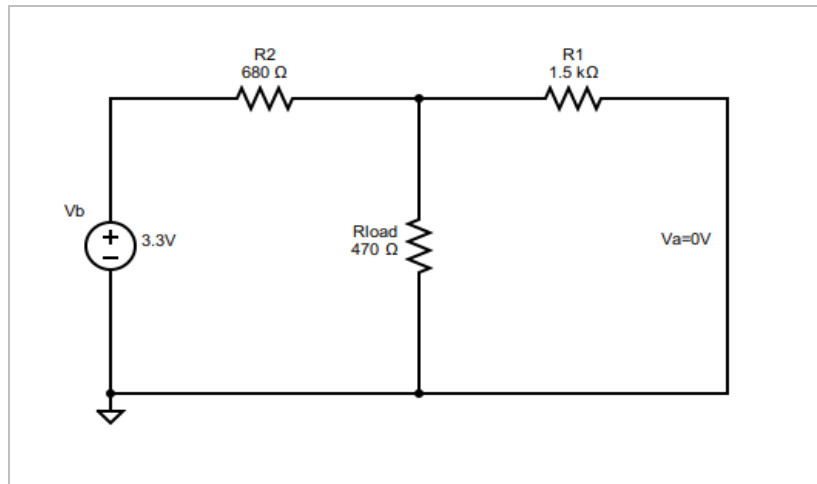


Figure 4: Vb acting alone

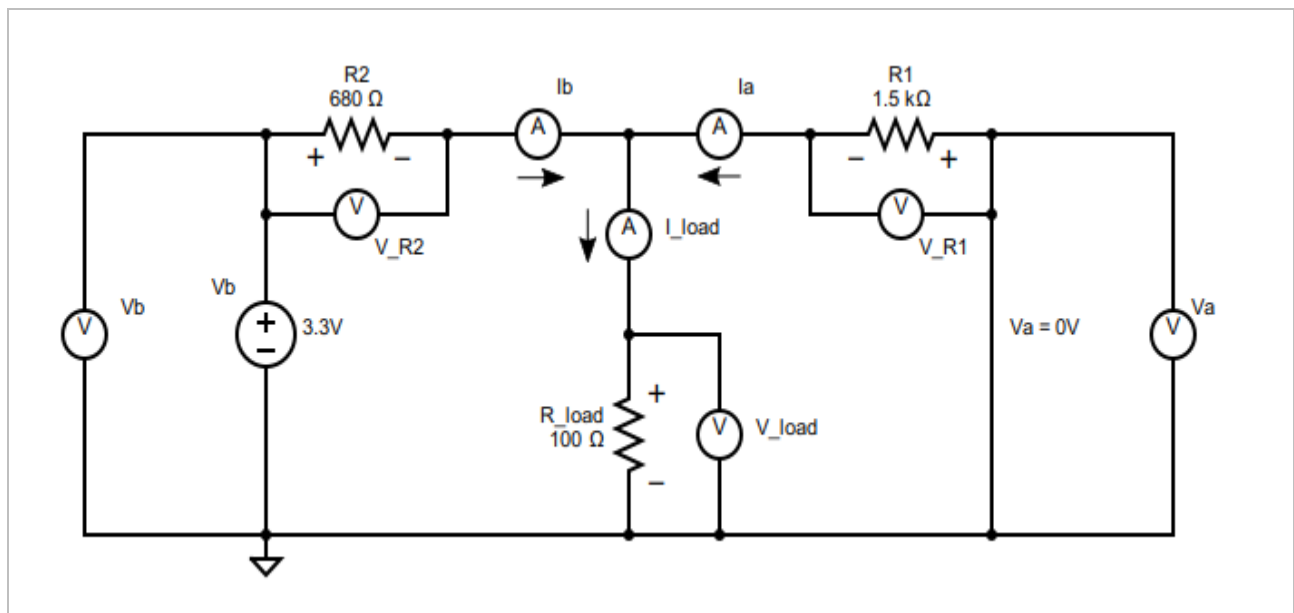

Circuit 4: Vb acting alone circuit (showing meter placement)

- a. Make the following changes to the circuit from the previous step:
 - Remove the Va voltage source from the circuit and replace it with a jumper wire to create a short circuit where the source once was. This is as easy as taking the one end of the red wire, from the test circuit breadboard diagram above, that is connected to V+ and moving it to Gnd.
- b. Enable the Vb source and make all the same measurements as you did with the previous test circuit again with all of the different values of R_load. Make sure to record all your measurements on the results sheet.
- c. After the completion of this section just turn off the Vb voltage source as you will continue to use this circuit in the next section.

2.3.2 V_a Acting Alone

5. Now test for the second source in the circuit independently; configure the test circuit to see how the circuit responds when only supplied by V_a .


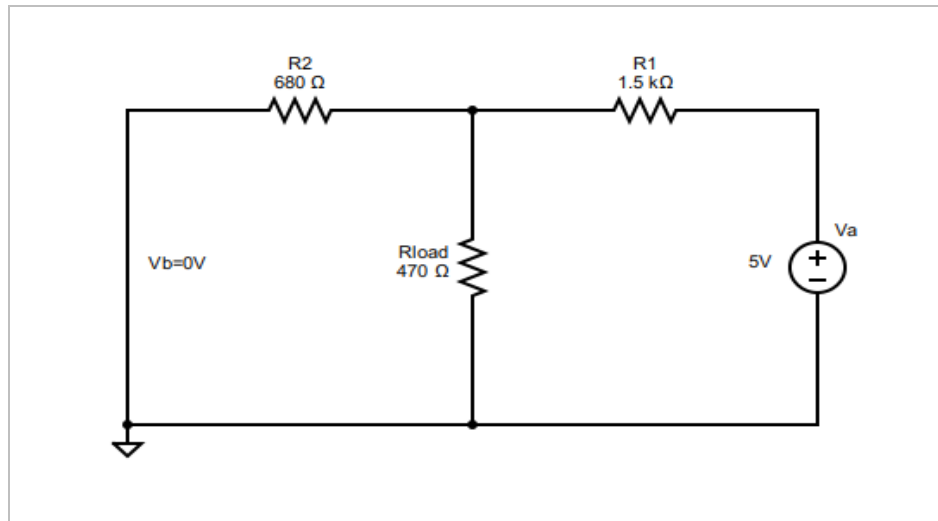


Figure 5: V_a acting alone

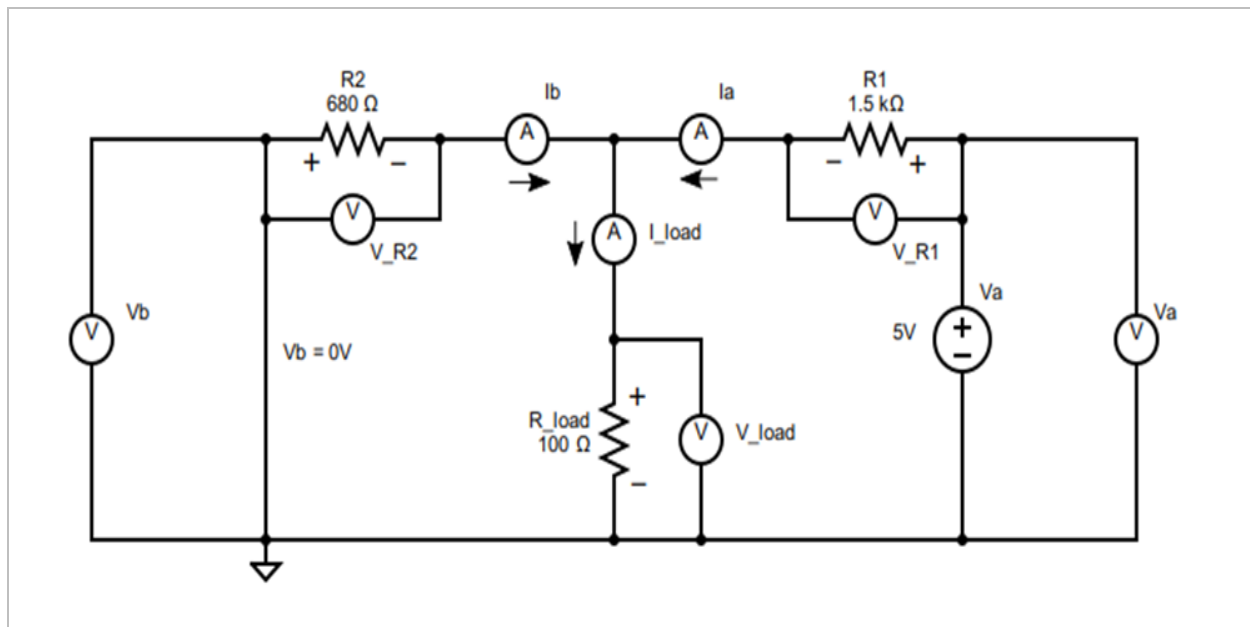

Circuit 5: V_a acting alone circuit (showing meter placement)

- a. Make the following changes to the circuit from the previous step:
 - Reconnect the V_a voltage source to the circuit by reversing the connection you did in the previous step by moving the one end of the red wire back to the $V+$ input.
 - Remove the V_b voltage source from the circuit and replace it with a jumper wire to create a short circuit where the source once was. This is as easy as taking the

one end of the yellow wire, from the test circuit breadboard diagram above, that is connected to W1 and moving it to Gnd.


- b. Enable the V_a source and make all the same measurements as you did with the previous test circuit again with all of the different values of R_{load} . Make sure to record all your measurements on the results sheet.
- c. After the completion of this section just turn off the V_b voltage source as you will continue to use this circuit in the Equivalent Parameters section.

2.4 Thevenin and Norton Theorems

2.4.1 Equivalent Parameters

2.4.1.1 Finding Thevenin-Equivalent Voltage

6. The circuit below demonstrates how to obtain the Thevenin Voltage for The Test Circuit as seen from R_{load} . To obtain the Thevenin Voltage the idea is to replace R_{load} with an open circuit and then measure the voltage across that open circuit. The circuit below is identical to the circuits used in the previous sections with only a couple of differences: All of voltmeters and ammeters have been removed and the resistor R_{load} has been replaced by a voltmeter.

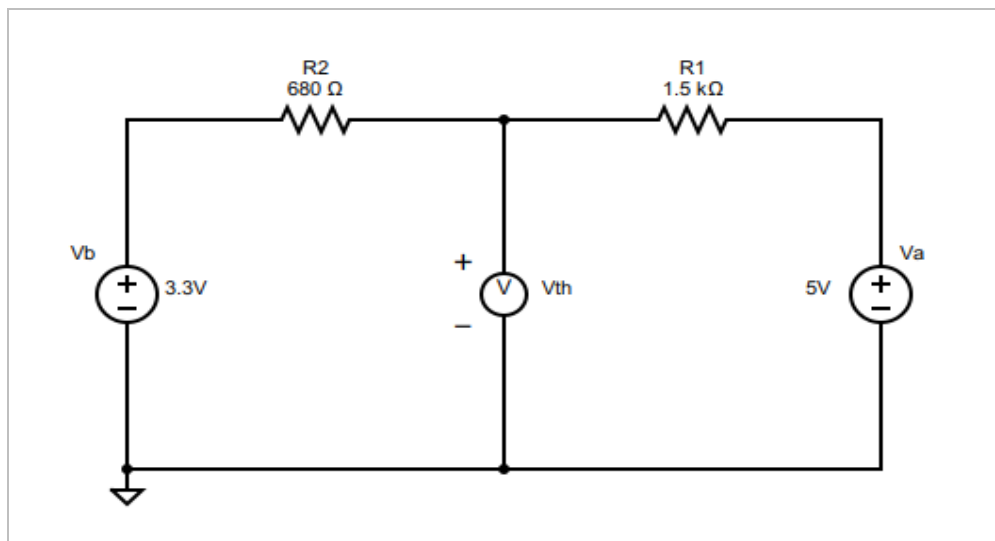


Circuit 6: Thevenin voltage circuit

- a. Make the following changes to the circuit from the previous step:
 - Reconnect the V_b voltage source to the circuit by reversing the connection you did in the previous step by moving the one end of the yellow wire back to the W1 input.
 - Remove all of the voltmeters and ammeters from the circuit.

- Remove the resistor R_{Load} from the circuit and replace it with a DC voltmeter of your choosing (either the Analog Discovery 2 or the DMM). By placing the voltmeter where R_{load} would normally go creates an open circuit in that location as voltmeters typically have a very large input resistance.
- b. Enable both voltage sources (V_b and V_a) and the value measured on the voltmeter will be the Thevenin equivalent voltage. Record this measurement on your results sheet.
- c. After you obtain your Thevenin Voltage just turn off both voltage sources (V_b and V_a) as you will continue to use this circuit.

2.4.1.2 Finding Norton Equivalent Current

7. The circuit below demonstrates how to obtain the Norton Current for The Test Circuit as seen from R_{load} . To obtain the Norton Current the idea is to now replace R_{Load} with a short circuit and then measure the current going through that short circuit.

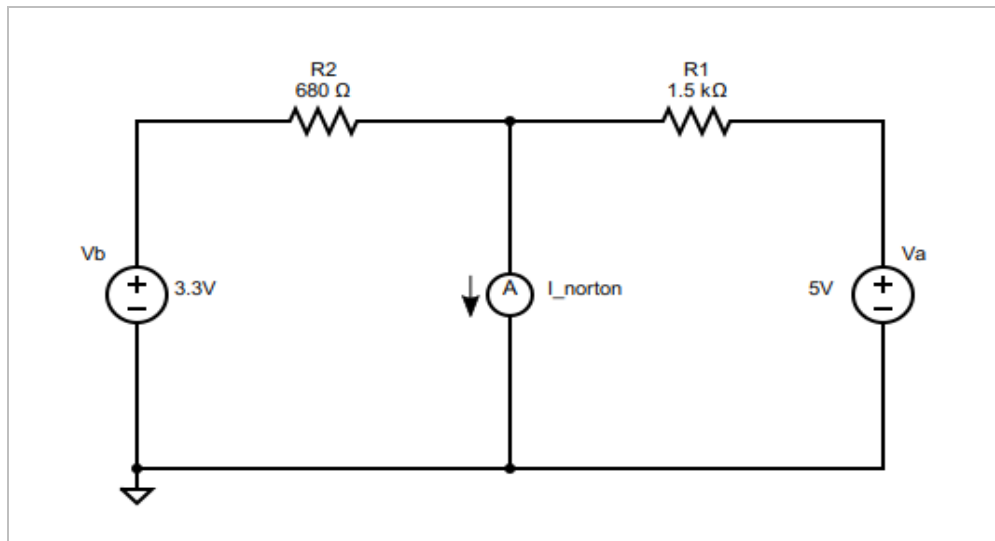

Circuit 7: Norton current circuit

- a. Make the following changes to the circuit from the previous step:
 - Remove the voltmeter that you used to measure the Thevenin voltage and replace it with the DMM configured as a milliammeter. By placing the milliammeter where R_{load} would normally go creates a short circuit in that location as ammeters typically have a very small near 0 Ω input resistance.
- b. Enable both voltage sources (V_b and V_a) and the value measured on the milliammeter will be the Norton equivalent current. Record this measurement on your results sheet.
- c. After you obtain your Norton Current just turn off both voltage sources (V_b and V_a) as you will continue to use this circuit.

2.4.1.3 Finding Thevenin/Norton Equivalent Resistance

8. The circuit below demonstrates how to obtain the Thevenin/Norton Resistance for The Test Circuit as seen from R_load using the 3rd method described below.


Note: Determining Thevenin/Norton Resistance

There are 3 common ways to determine this resistance:

- i. By dividing the Thevenin-equivalent voltage by the Norton-equivalent current found in the previous steps.

$$R_{TH} = R_{NORTON} = \frac{V_{TH}}{I_{NORTON}} \quad (1)$$

- ii. By changing the resistance of R_load until the voltage across R_load is equal to half of the Thevenin-equivalent voltage. At this operating point the value of R_load is equivalent to R_TH and R_NORTON.
- iii. By replacing all of the sources with its internal resistance (i.e. shorting all voltage sources and opening all current sources) and measuring the resistance at the terminals.

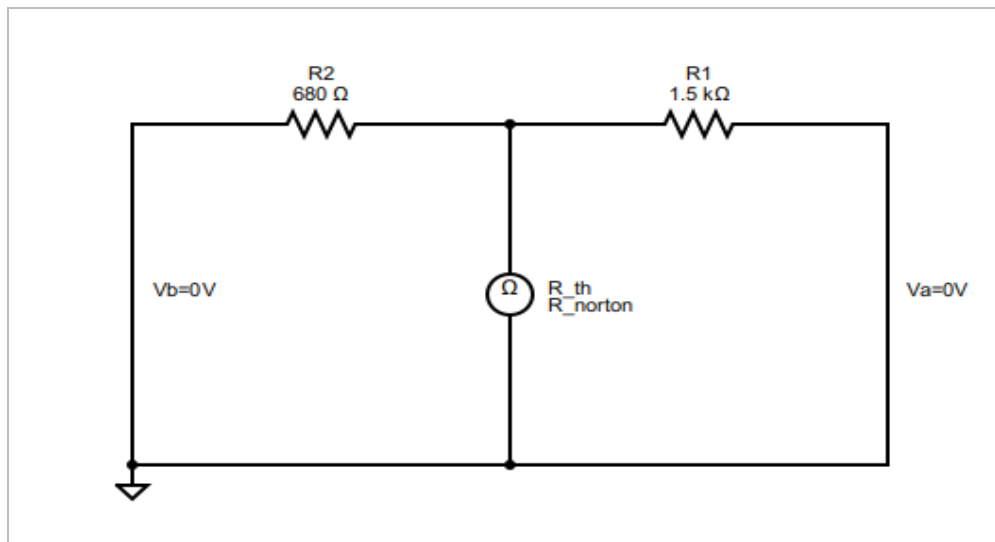

Circuit 8: Thevenin and Norton resistance circuit

- a. Make the following changes to the circuit from the previous step:
 - Remove both the Vb and Va voltage sources from the circuit and replace them with jumper wires to create a short circuit where the sources once were.
 - With the DMM still connected in the location of R_load rotate the DMM dial to the ohmmeter setting.
- b. The value measured on the ohmmeter will be the Thevenin/Norton equivalent resistance. Record this measurement on your results sheet.


- c. At this point double check your results to make sure you have everything required in the results sheet up to this point and that the measurements make sense to you. You can now disconnect this entire breadboard circuit as you will not need it anymore.

2.4.2 Thevenin Circuit

Thevenin's Theorem

Thevenin's Theorem states that any linear electrical network as seen from 2 nodes can be simplified to an equivalent circuit with just a single voltage source (V_{TH}) in series with a resistance (R_{TH}) and then connected to the load.

9. To demonstrate that the Thevenin equivalent circuit behaves the same as The Test Circuit as seen from R_{load} , connect the circuit below using the equivalent parameters you found in your tests from the previous section.

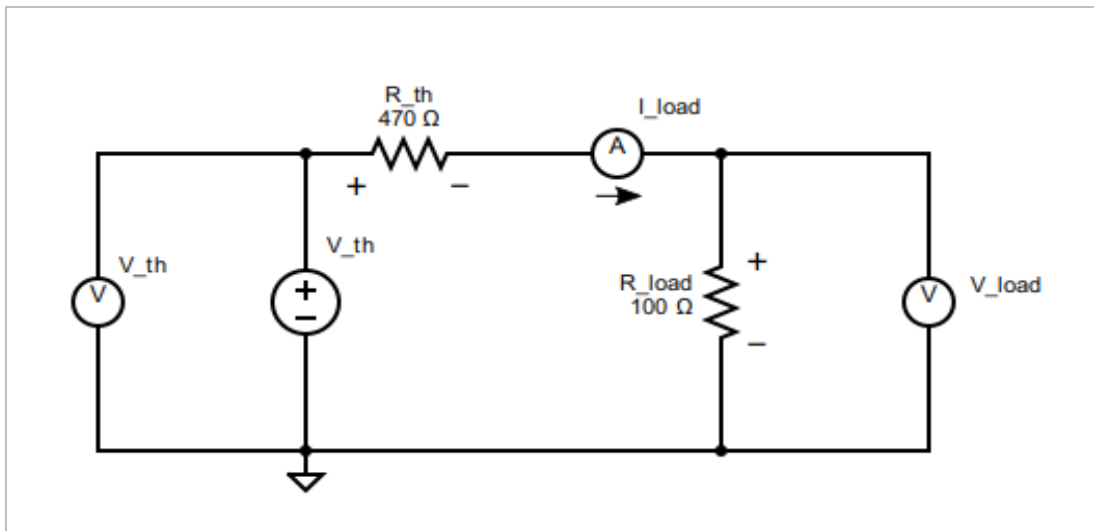

Circuit 9: Thevenin circuit

- a. Connect the circuit above using the following:
- You can just use a single 470Ω as the Thevenin resistor (R_{th}) as it should fall within the tolerance of the desired resistance. Before placing the resistor in the circuit measure it using the DMM as an ohmmeter and record the measurement on the results sheet.
 - Use the positive DC voltage source ($V+$ and Gnd) from the Analog Discovery 2 as V_{th} . Set it to Thevenin equivalent voltage determined in the previous section.
 - Measure the current (I_{load}) using the DMM as a milliammeter.
 - Measure the voltage (V_{th}) using channel 1 (1+ and 1-) of the 'Voltmeter' on the Analog Discovery 2.


- Measure the voltage (V_{load}) using channel 2 (2+ and 2-) of the 'Voltmeter' on the Analog Discovery 2.
 - Start by using a 100Ω resistor for the value of R_{load} . You will switch out this load resistor a few times for another value when required.
- Enable the appropriate DC voltage source in Waveforms and measure V_{th} , V_{load} and I_{load} and record it on the results sheet for this value of $R_{load} = 100\Omega$.
 - Change the load resistor (R_{load}) the same way you did for The Test Circuit to different values one at a time (220Ω , 470Ω , $1.0k\Omega$ and $2.2k\Omega$). Measure and record V_{load} and I_{load} on the results sheet for each load resistor.
 - After turning your voltage sources off you can now disconnect this entire breadboard circuit as you will not need it anymore.

2.4.3 Norton Circuit

Norton's Theorem

Norton Theorem states that any linear electrical network as seen from 2 nodes can be simplified to an equivalent circuit with just a single current source (I_{NORTON}) and parallel resistance (R_{NORTON}) connected to the load.

- To demonstrate that the Norton equivalent circuit behaves the same as both the Thevenin Circuit and The Test Circuit as seen from R_{load} , connect the circuit below using the equivalent parameters you found in your tests from the previous section.

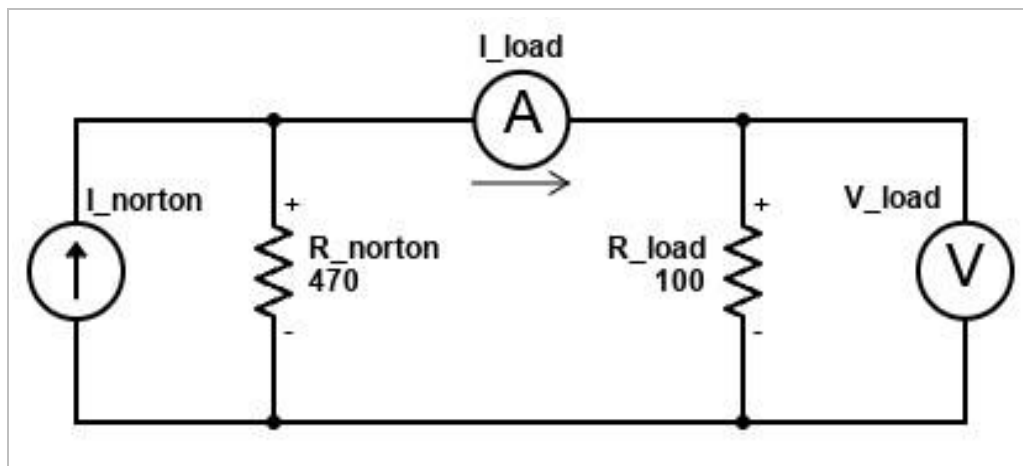

Circuit 10: Norton circuit

- First connect and test the current source by connecting the following:
 - The LM234Z current source. (To get more information please go through datasheet given in section 1.2)

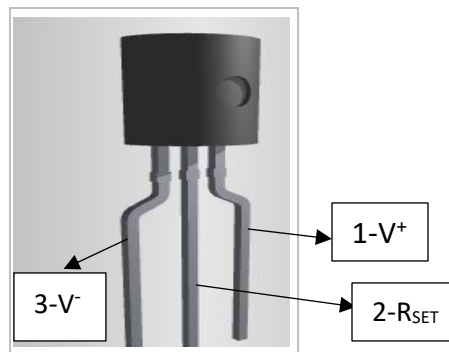


Figure 6: LM234Z current source 3D model

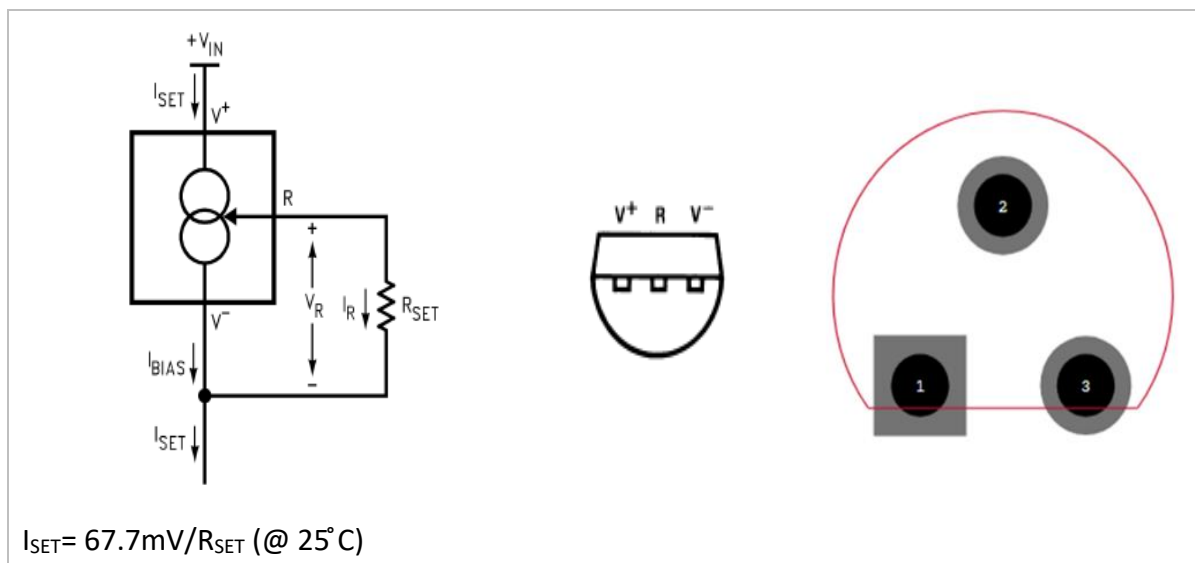


Figure 7:LM234Z (Left: as a basic current source, Middle: bottom view, Right: foot print)

- Connect terminal 1 (V^+) of LM234Z to V^+ of the Analog Discovery 2.
 - Connect an $8.3\ \Omega$ ($4.7\ \Omega + 3.6\ \Omega$) resistor as R_{SET} at the middle terminal of the LM234Z. (To get an $8.3\ \Omega$ resistor, you need to connect $4.7\ \Omega$ and $3.6\ \Omega$ resistors in series as shown in figure 8.)
 - As indicated in figure 8, the other end of the $8.3\ \Omega$ ($4.7\ \Omega + 3.6\ \Omega$) resistor (R_{SET}) and terminal 3(V^-) must be connected together with the use of the jumper wires.
 - Connect the red probe of the DMM configured as a milli-ammeter to the I_{SET} point in the diagram above. Connect the black probe of the DMM to the V^- of the analog discovery2.
- b. Your circuit should look something like this when completed.

2.4.4 Thevenin-Norton Equivalency

Source Transformations

Performing a source transformation consists of using Ohm's law to take an existing voltage source in series with a resistance, and replacing it with a current source in parallel with the same resistance, or vice versa. The transformed sources are considered identical and can be substituted for one another in a circuit.

Norton → Thevenin conversion

$$V_{th} = I_{norton} \times R_{norton} \quad (2)$$

$$R_{th} = R_{norton} \quad (3)$$

Thevenin → Norton conversion


$$I_{norton} = \frac{V_{th}}{R_{th}} \quad (4)$$

$$R_{norton} = R_{th} \quad (5)$$

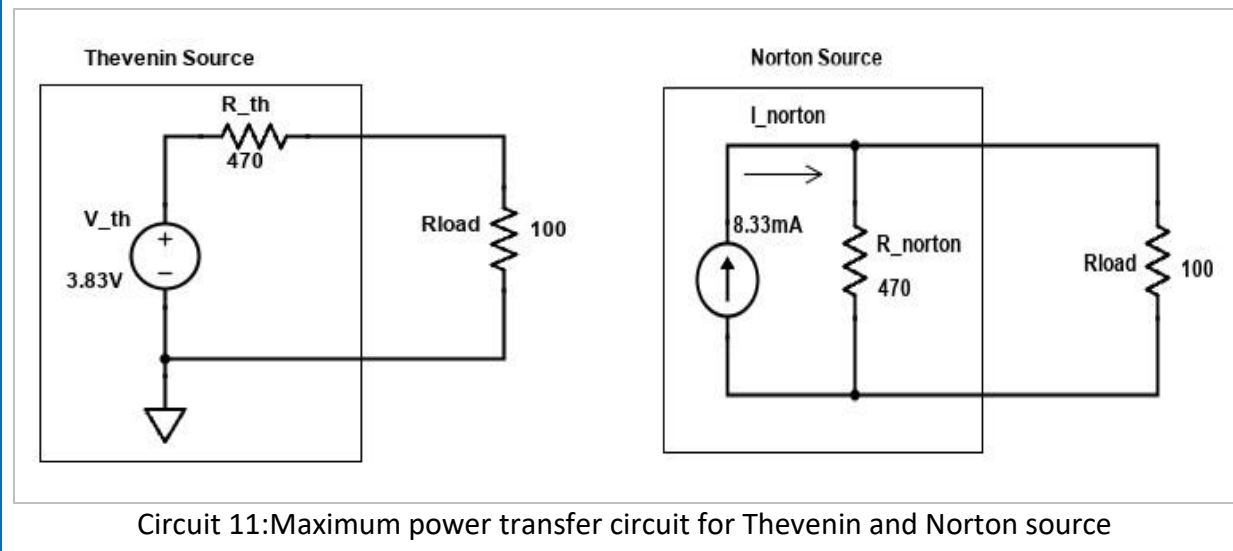2.5 Maximum Power Transfer

Maximum Power Transfer

The Maximum Power Transfer Theorem states that the maximum amount of power will be dissipated by a load resistance if it is equal to the Thevenin or Norton resistance of the network supplying power. The Maximum Power Transfer Theorem does not satisfy the goal of maximum efficiency.



2.6 Cleanup

Congratulations, you have completed the experimental part of the laboratory. Verify your results with a lab instructor or TA before cleaning up. If you are not continuing to work with the equipment please disconnect everything and put it away to prevent it from getting damaged.

3 Post Lab

The following is what you are expected to complete & submit for grading of Lab 2 before the deadline.

1. The Lab 2 - Results sheet is provided on lab eClass page. This sheet should include the following.
 - Your name, student ID and CCID.
 - All of the required measurements from the lab procedures.
 - Answer the questions available on a Lab 2 result sheet.
 - All of the required calculations as discussed below.
 - The required plots as discussed below.
2. The **Lab2 - Result Sheet** needs to be submitted to the Submit (**Lab 2 - Results**) link on eClass as a **PDF** document. Only one lab report is required to be submitted per group. Information regarding the due date of Lab 2 report submission is available on eClass lab schedule.
3. Complete the online **Quiz (Lab 2 - Post Lab)** on eClass individually, which will be due usually on same day as a lab result sheet. Detailed Information regarding the due date of Lab 2 Quiz is available on eClass lab schedule.

3.1 Calculations

For these calculations you only need to provide the answers in the space provided on your results sheet, you do not need to show your work other than requested on the result sheet.

- i. For the Delta-Wye Transformations under Wye use the Delta-Wye transformation equations to calculate the equivalent Wye values for R_1 , R_2 and R_3 from the measured Delta resistance values R_a , R_b and R_c .
- ii. From your calculated values of R_1 , R_2 and R_3 from the previous step, calculate what the resistance between the terminals labelled u-v, v-w and w-u should be.
- iii. For the Delta-Wye Transformations under Delta use the Wye-Delta Transformation equations to calculate the equivalent Delta values for R_a , R_b and R_c from the measured Wye resistance values R_1 , R_2 and R_3 .

- iv. From your calculated values of R_a , R_b and R_c from the previous step, calculate what the resistance between the terminals labelled x-y, y-z and z-x should be.
- v. For Superposition complete the Superposition (V_b Acting Alone + V_a Acting Alone) by summing the values of each cell in the V_b Acting Alone table with the corresponding cell in the V_a Acting Alone table.
- vi. For the Thevenin Circuit calculate the power supplied by the voltage source (P_{source}) and the power dissipated by the load (P_{load}) for each value of R_{load} . Then calculate the overall efficiency of the circuit.
- vii. For the Norton Circuit calculate the power supplied by the current source (P_{source}) and the power dissipated by the load (P_{load}) for each value of R_{load} . Then calculate the overall efficiency of the circuit.

3.2 Plots

To create your plots you can use whichever software you would like (Excel, Matlab, etc), export your plot as an image and import it into your Lab 2 - Results sheet in the appropriate place.

Your plots should include:

- A Plot title
 - Label your axes and show what unit of measure is used.
 - Include a marking for your datapoints.
 - Include a line between your datapoints in the same series.
 - Include a legend.
 - Make sure your scales are appropriate and visible.
- i. **Characteristic Plot:** For each of these 3 circuits: The Test Circuit, Thevenin Circuit and Norton Circuit plot the load current vs. load voltage on the same plot.
 - ii. **Thevenin Circuit Plot:** Plot the load power vs. load resistance as one series and the circuit efficiency vs. load resistance as a second series using a secondary y-axis scale.
 - iii. **Norton Circuit Plot:** Plot the load power vs. load resistance as one series and the circuit efficiency vs. load resistance as a second series using a secondary y-axis scale.